
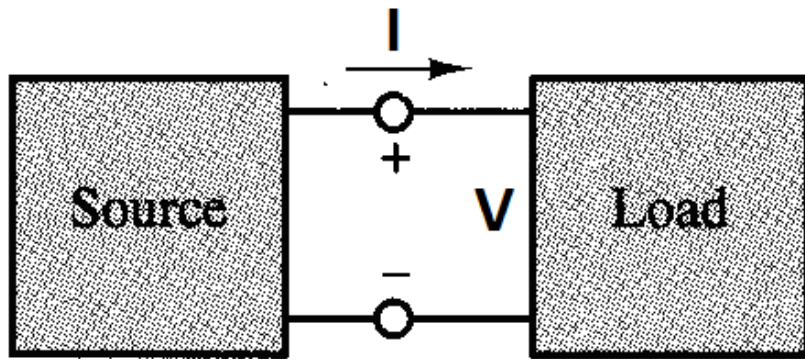


# Thevenin vs. Norton


謝志誠

最新更新：2012年4月11日

**Thevenin  
Equivalent Circuit**

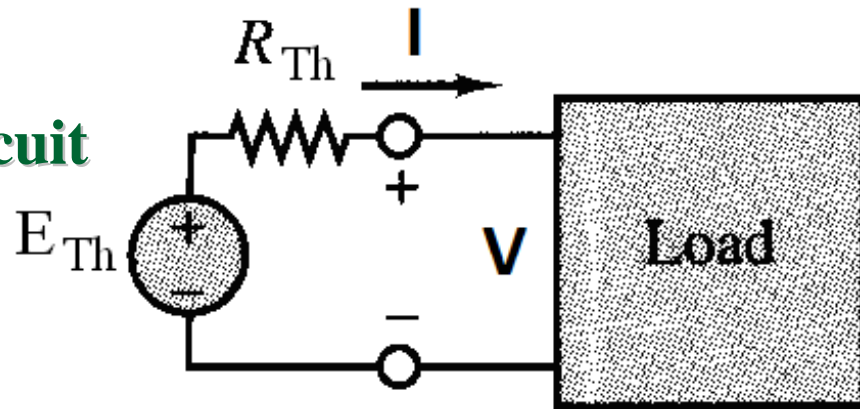


**Norton  
Equivalent Circuit**

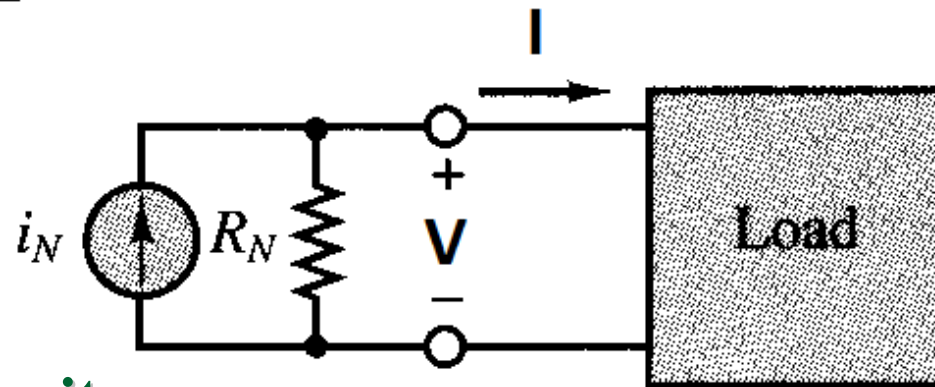

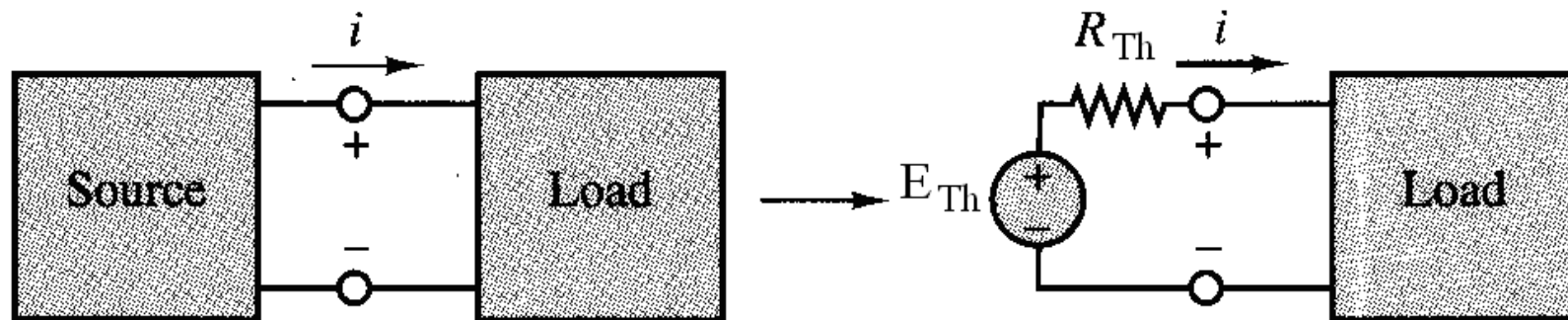
# Thevenin theorem

- 戴維寧定理又稱等效電壓源定律，是由法國科學家 Thevenin 於 1883 年提出的一個電學定理。
- 一個接於兩點間，含有獨立電壓源、獨立電流源及電阻的線性電路，就其外部型態而言，在電性上可以用一個獨立電壓源  $E_{Th}$ （戴維寧等效電壓）和一個串聯的電阻  $R_{Th}$ （戴維寧等效電阻）組合來等效。



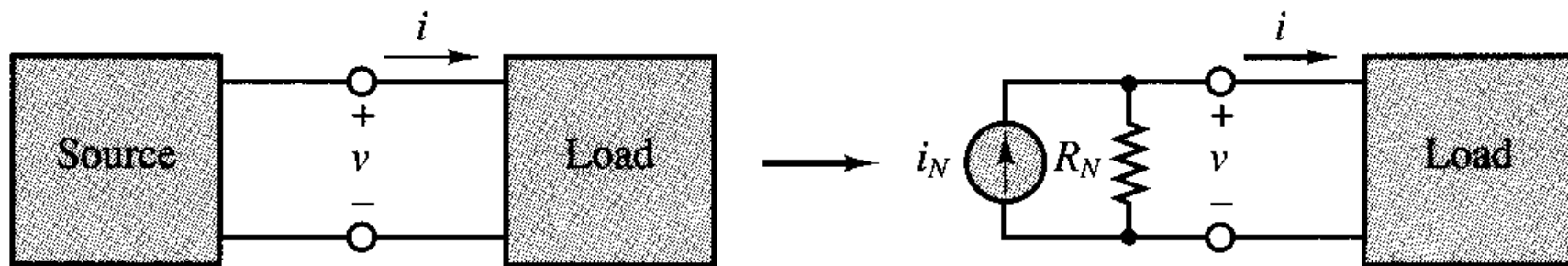
# Norton theorem

- 諾頓定理是戴維寧定理的一個延伸，於1926年由Hause-Siemens研究員漢斯·費迪南·梅耶爾及貝爾實驗室工程師愛德華·羅里·諾頓分別提出。
- 一個接於兩點間，含有獨立電壓源、獨立電流源及電阻的線性電路，就其外部型態而言，在電性上可以用一個獨立電流源 $I_n$ （諾頓等效電流）和一個並聯的電阻 $R_N$ （戴維寧等效電阻）組合來等效。


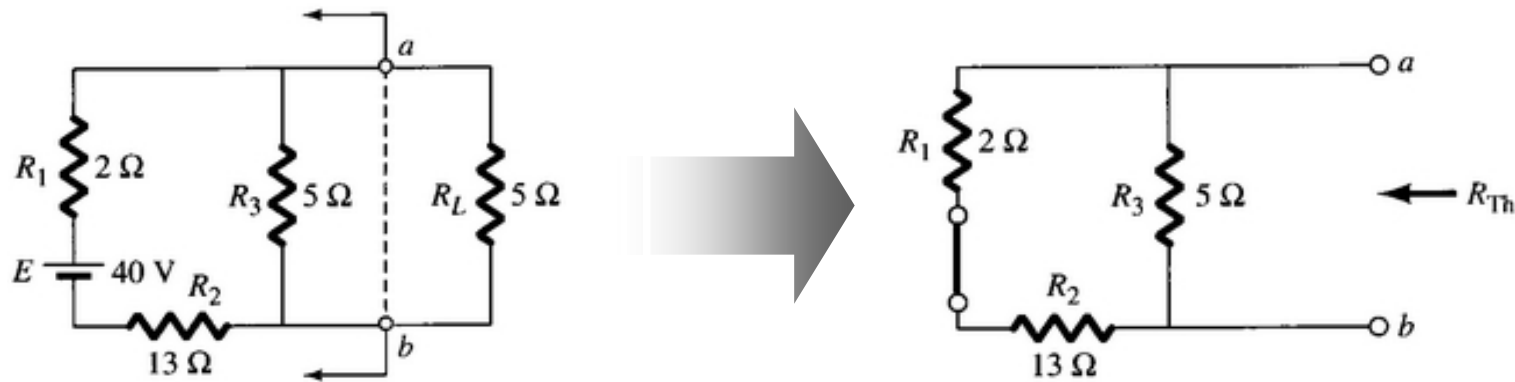
# $R_{Th}$



- 將欲探討的支路上的元件（負載）移走，成為開路。
- 將電路中所有的**電壓源短路**，**電流源開路**，求元件移走後電路兩端的等效電阻 $R_{Th}$ 。




$$R_{Th} = R_3 \parallel (R_1 + R_2) = \frac{(5 \Omega)(15 \Omega)}{5 \Omega + 15 \Omega} = 3.75 \Omega$$
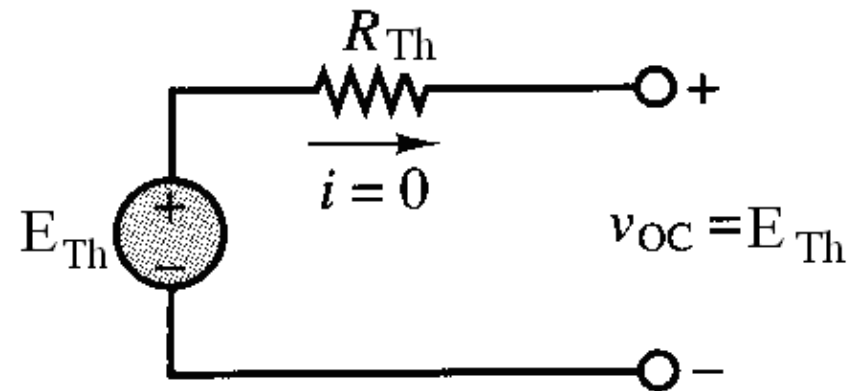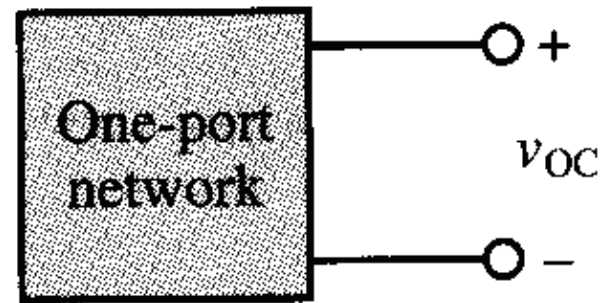
# $E_{Th}$ 1/2

- 將電壓源、電流源置回原處，再應用各種解電路的方法求出元件移走後，電路兩端的電壓，即為等效電壓 $E_{Th}$ 。




# $E_{Th}$ 2/2

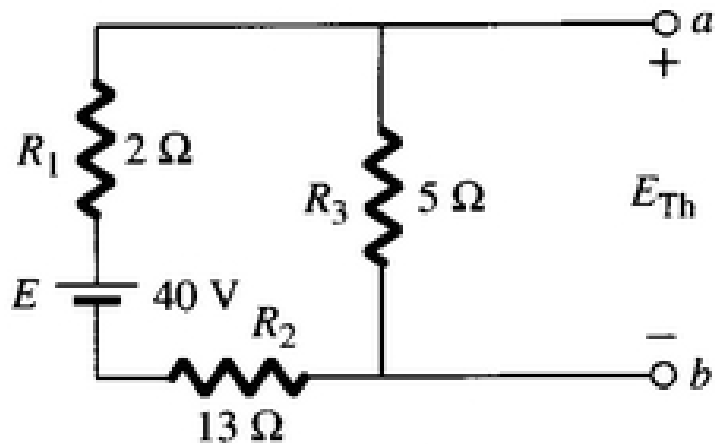

$$E_{Th} = V_{R_3} = \frac{R_3 E}{R_T} = \frac{(5 \Omega)(40 \text{ V})}{20 \Omega} = \frac{200 \text{ V}}{20} = \mathbf{10 \text{ V}}$$

即使改變負載，也很容易  
計算改變後的電流多！

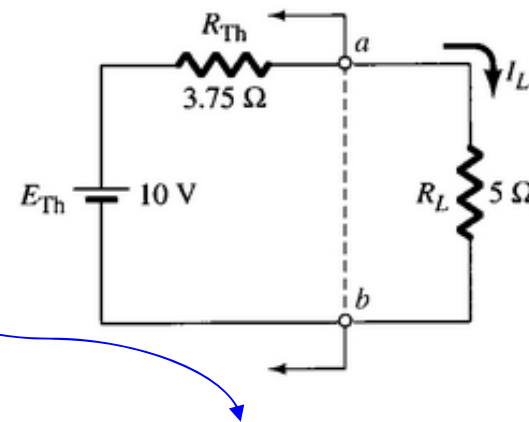
$$I_L = \frac{E_{Th}}{R_{Th} + R_L} = \frac{10 \text{ V}}{3.75 \Omega + 30 \Omega} = \mathbf{0.296 \text{ A}}$$



$$I_L = \frac{E_{Th}}{R_{Th} + R_L} = \frac{10 \text{ V}}{3.75 \Omega + 5 \Omega} = \mathbf{1.143 \text{ A}}$$

$$R_N = R_{Th}$$

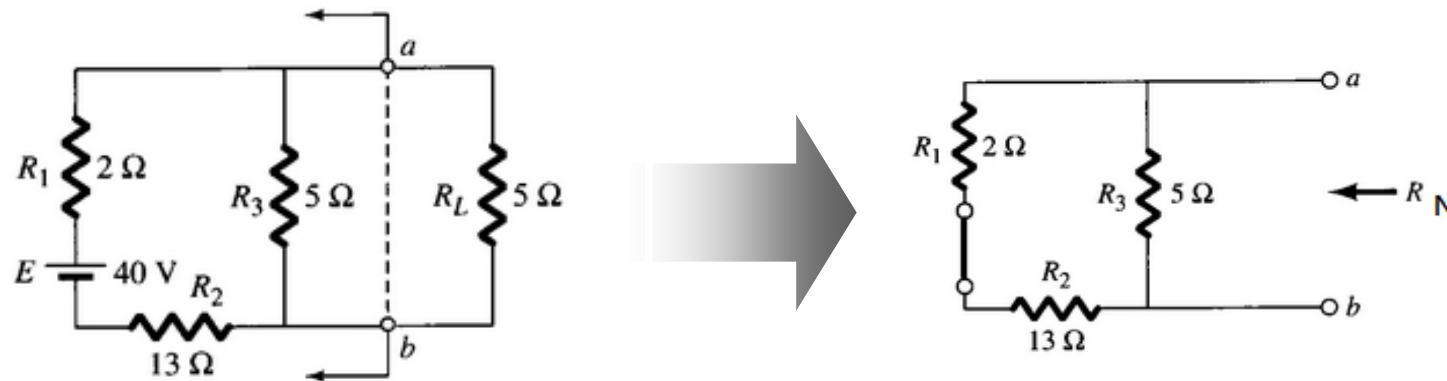- 將欲探討的支路上的元件（負載）移走，成為開路。
- 將電路中所有的**電壓源短路**，**電流源開路**，求元件移走後電路兩端的等效電阻 $R_N$ 。





$$R_N = (R_1 + R_2) // R_3 = 3.75\Omega$$




$i_N$  1/2

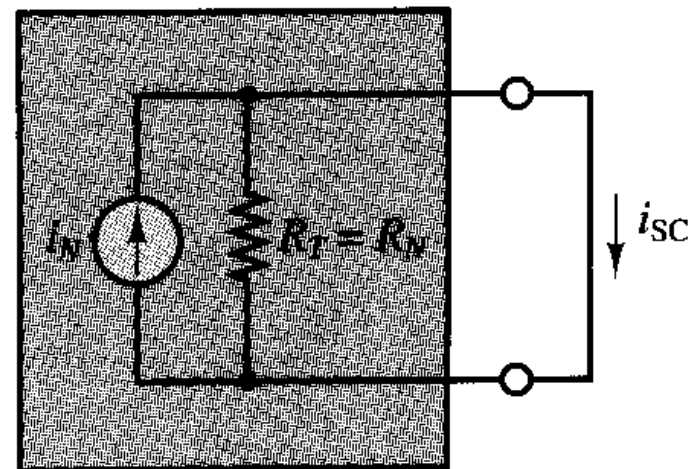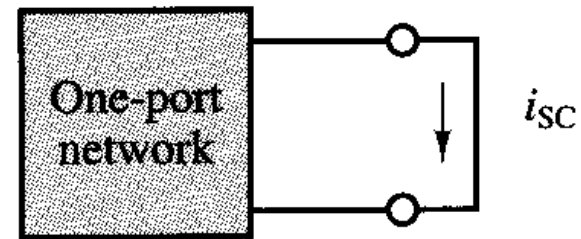
- 將電壓源及電流源放回  
去，且將移去的負載元件  
兩端設定為短路，再應用  
前述各種求解電路的方法，  
求出流過此短路線上的  
電流 $i_{SC}$ ，此電流即為  
等效電流 $i_N$ 。




$i_N$  2/2

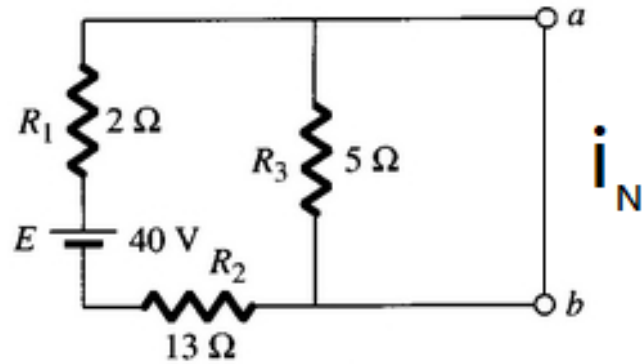
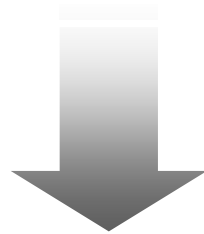
$$i_N = \frac{E}{R_1 + R_2} = \frac{40\text{V}}{15\ \Omega} = 2.667\text{A}$$



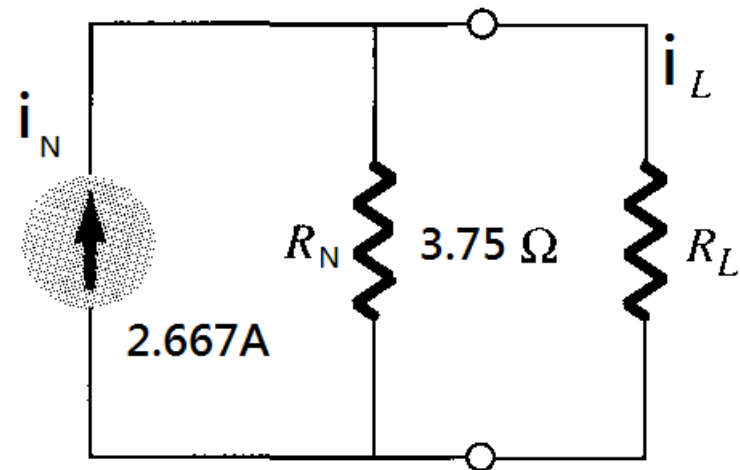
$$i_L = i_N \times \frac{R_N}{R_N + R_L} = 1.143\text{A}$$



# General Method

实验报告

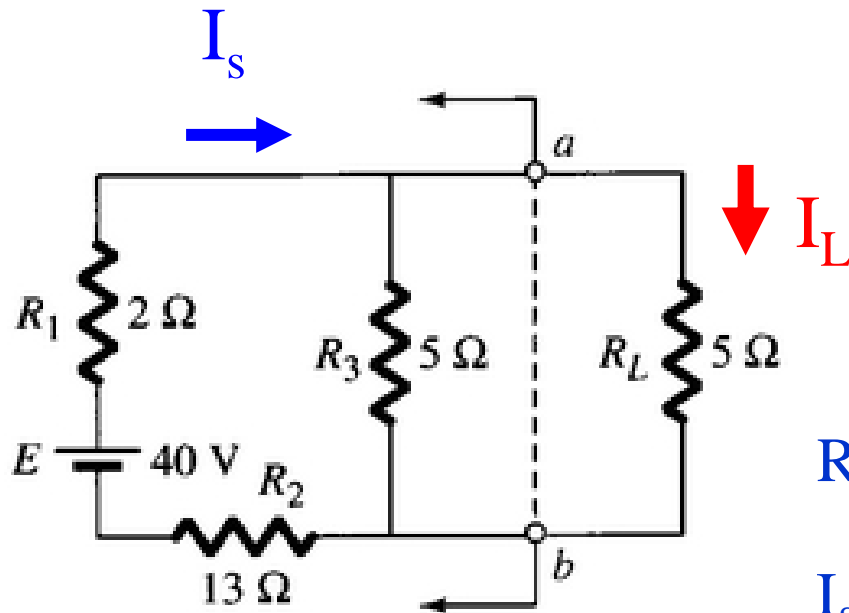




$$R_T = (R_L // R_3) + R_1 + R_2 = 17.5\Omega$$

$$I_S = \frac{E}{R_T} = 2.286\text{A}$$

$$I_L = I_S \times \frac{R_3}{R_3 + R_L} = 1.143\text{A}$$

# Source Conversion

张宇合

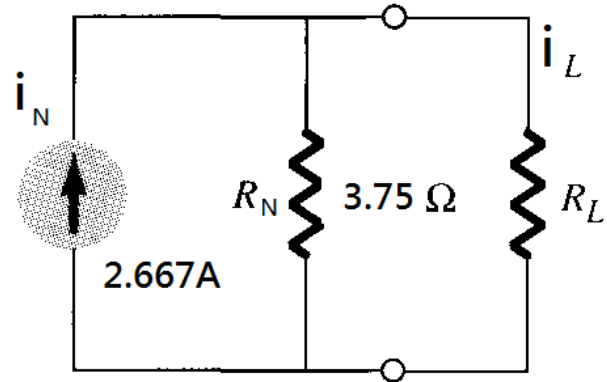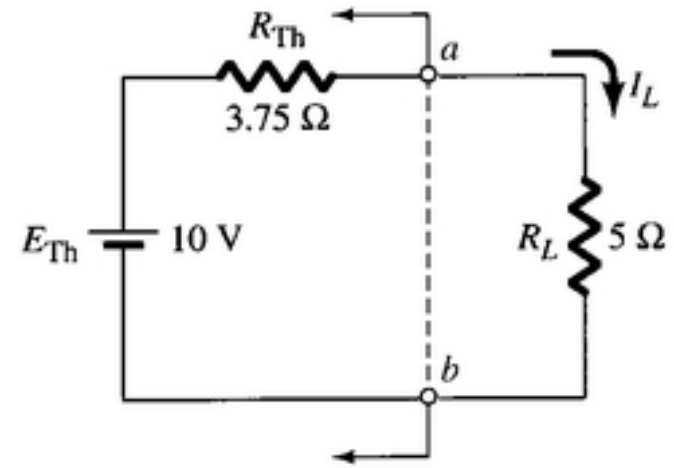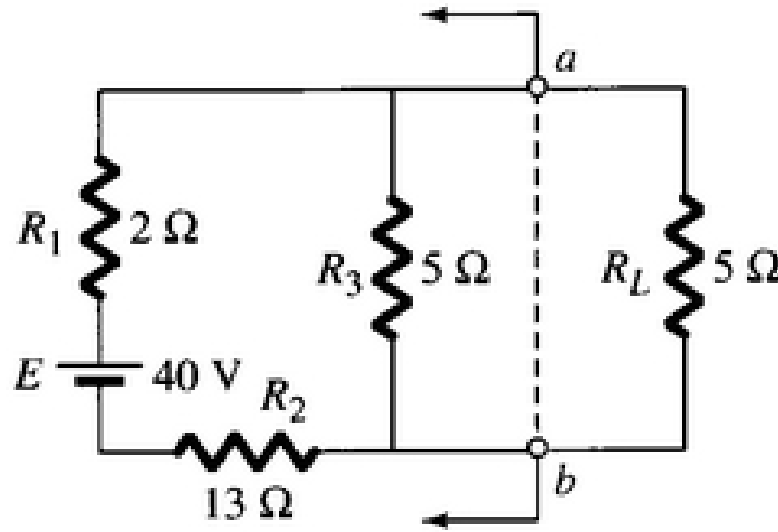


$$R_N = R_{Th}$$


$$i_N = \frac{E_{Th}}{R_{Th}}$$

$$E_{Th} = i_N \times R_N$$


# Application 1/2

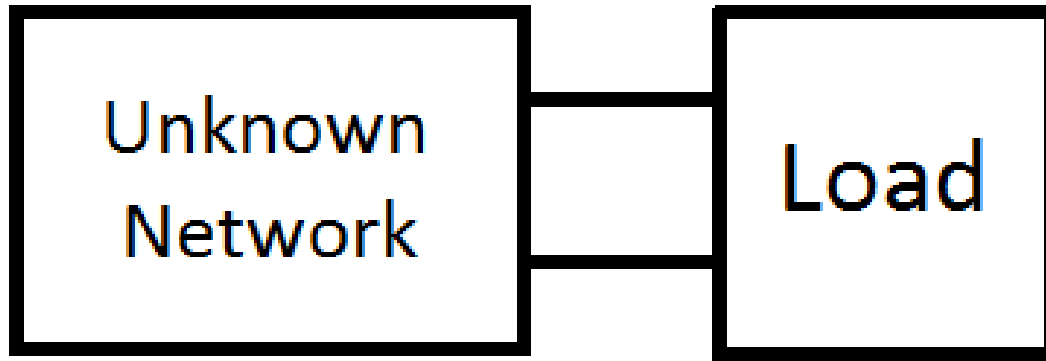


把未知電路表  
達成Thevenin  
與Norton等效？

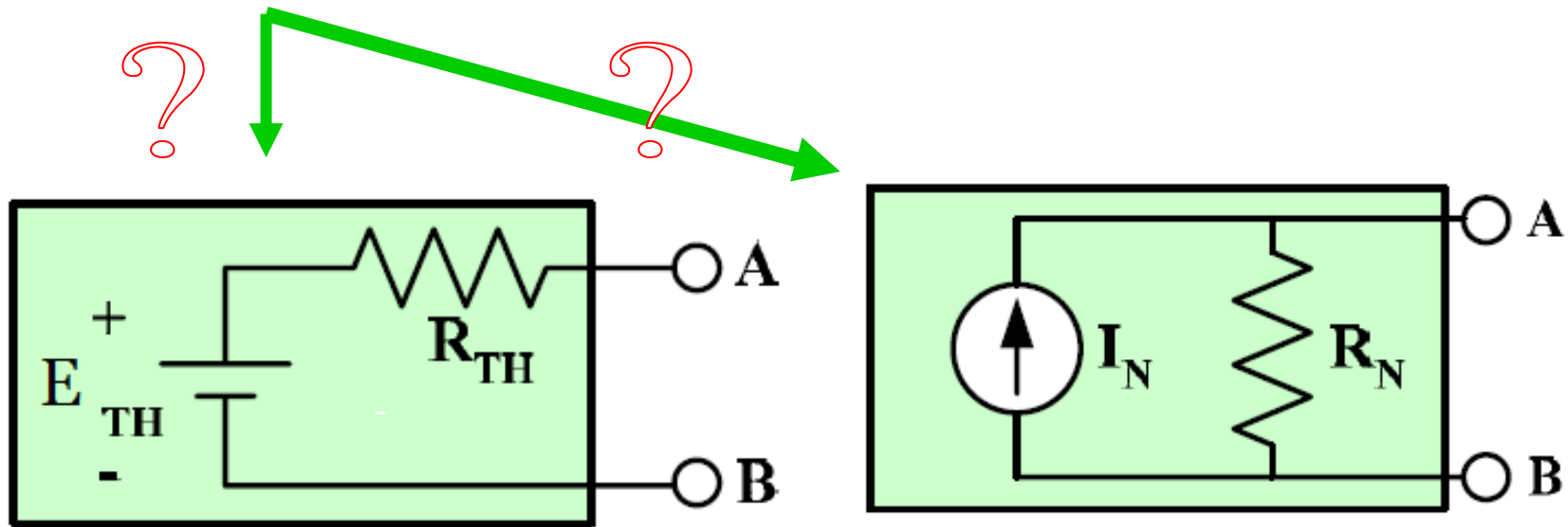

# Application 2/2

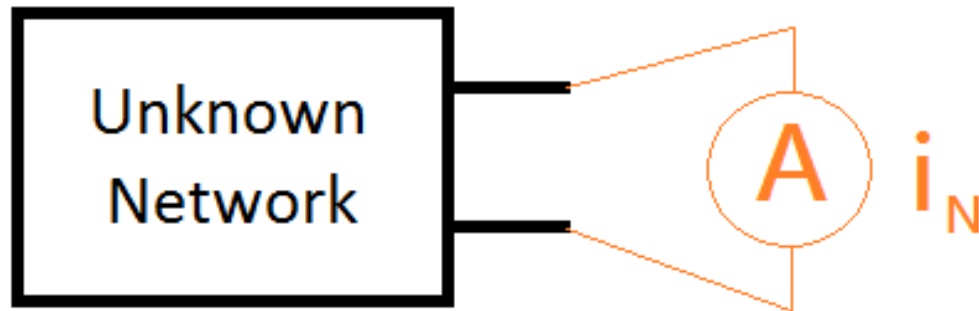


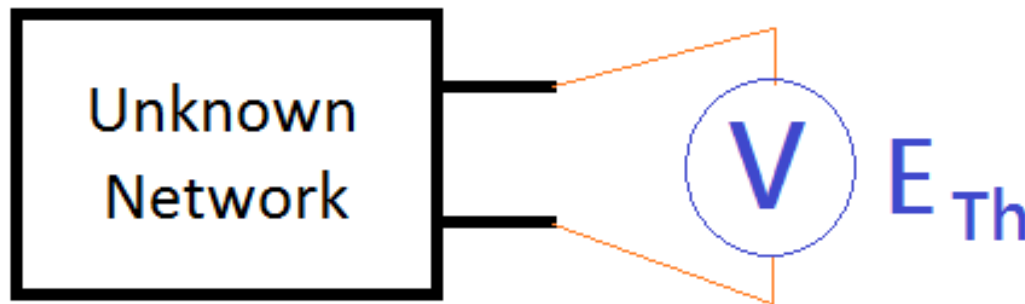延伸命題：如果使用的ammeter與voltmeter非理想儀器，而是有內部電阻時，結果又如何？




$$R_{TH} = R_N = E_{TH} \div I_N$$
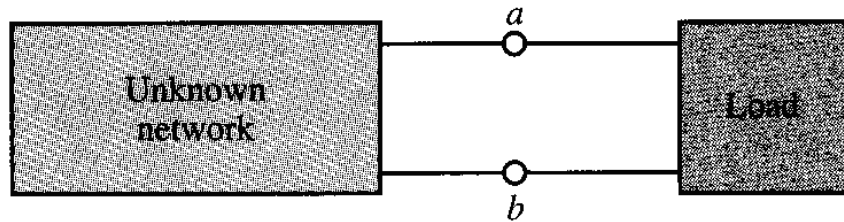
# Experimental Determination of Thevenin and Norton Equivalents




An unknown network connected to a load

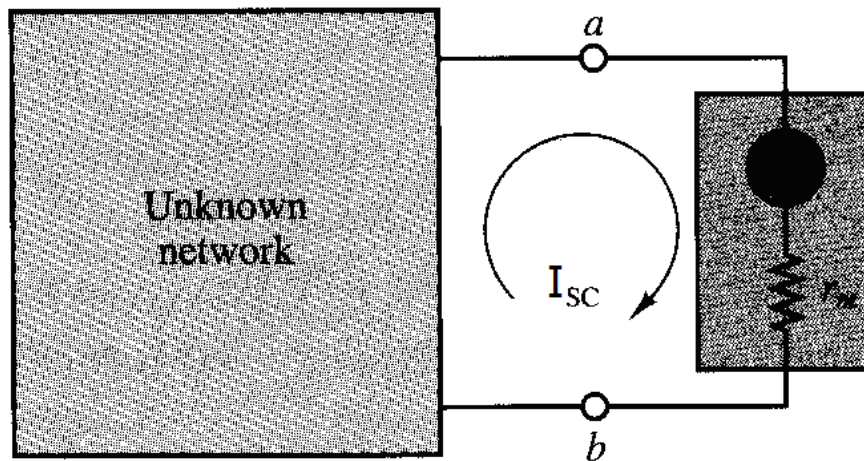


Network connected for measurement of short-circuit current

$$I_N = I_{SC} \left( 1 + \frac{r_m}{R_{TH}} \right)$$
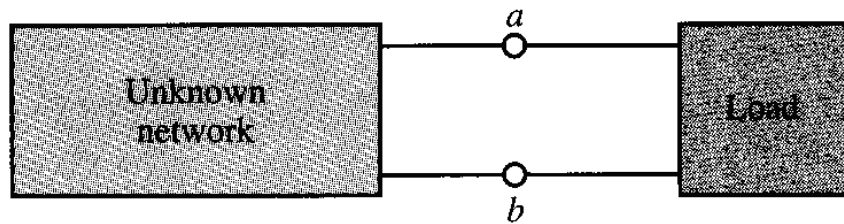
# Experimental Determination of Thevenin and Norton Equivalents



An unknown network connected to a load

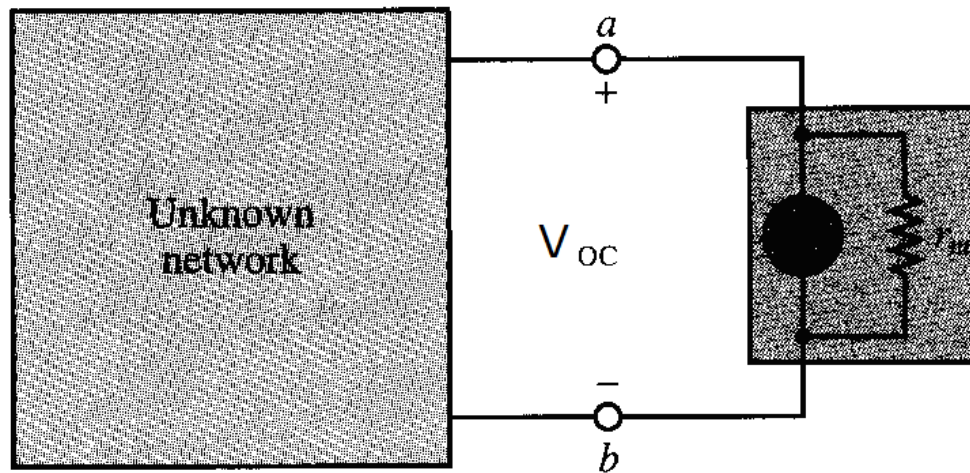

Network connected for measurement of open-circuit voltage

$$E_{TH} = V_{oc} \left( 1 + \frac{R_{TH}}{r_m} \right)$$



# Example

Measured  $V_{OC}=6.5V$


Measured  $I_{SC}=3.75mA$   $r_m=15\ \Omega$

**The unknown circuit is replaced by its Thevenin equivalent.**


$$E_{TH} = V_{OC} = 6.5V$$

$$I_N = I_{SC} \left( 1 + \frac{r_m}{R_{TH}} \right)$$
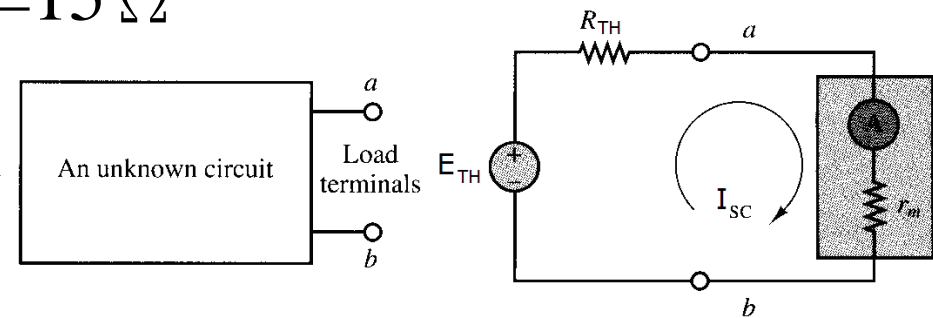
$$R_{TH} = \frac{E_{TH}}{I_N} = \frac{V_{OC}}{I_{SC}} - r_m$$



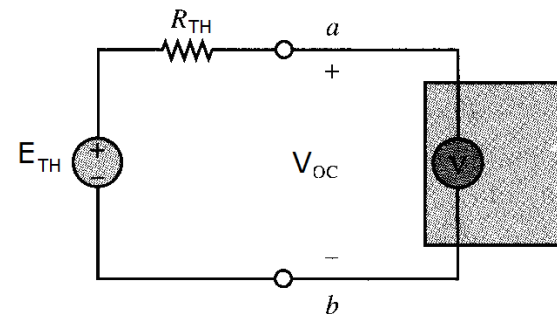Network connected for measurement of short-circuit current (practical ammeter)



Network connected for measurement of open-circuit voltage (ideal voltmeter)


# Maximum Power Transfer

- 確保負載可以從supply收到最多的功率！
- 當  $R_L = R_{Th}$  時，負載可以從supply收到最多的功率！

$$R_L = R_{Th}$$

$$I_L = \frac{E_{Th}}{R_L + R_{Th}} = \frac{E_{Th}}{2R_{Th}}$$
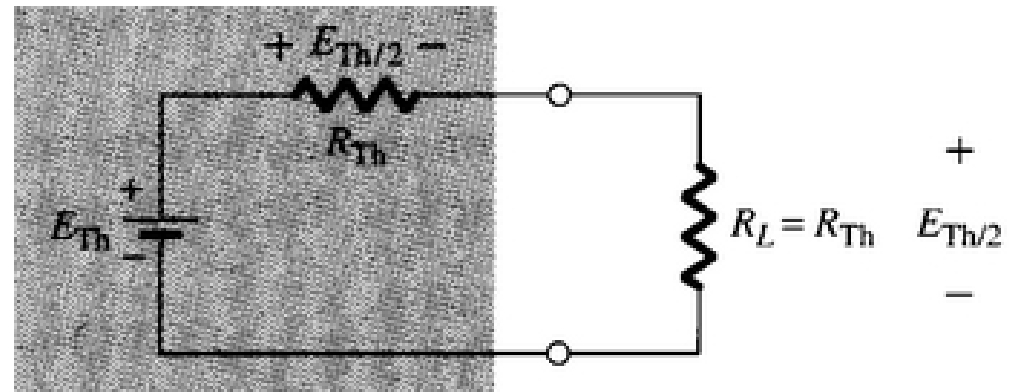
$$P_L = I_L^2 R = \left( \frac{E_{Th}}{2R_{Th}} \right)^2 R_{Th}$$



$$P_{Lmax} = \frac{E_{Th}^2}{4R_{Th}}$$

當  $R_L = 0.5R_{Th}$  或  $R_L = 1.5R_{Th}$ ，將發現Power都較低

# Exercise 20 Thevenin network

20. a. Find the Thévenin network for the portion of the network in Fig. 3.89 to the left of resistor  $R_L$ .
- b. Using the Thévenin network, determine  $I_L$ .
- c. Use series–parallel techniques on the original network to determine  $I_L$ , and compare the results with those for part (b).


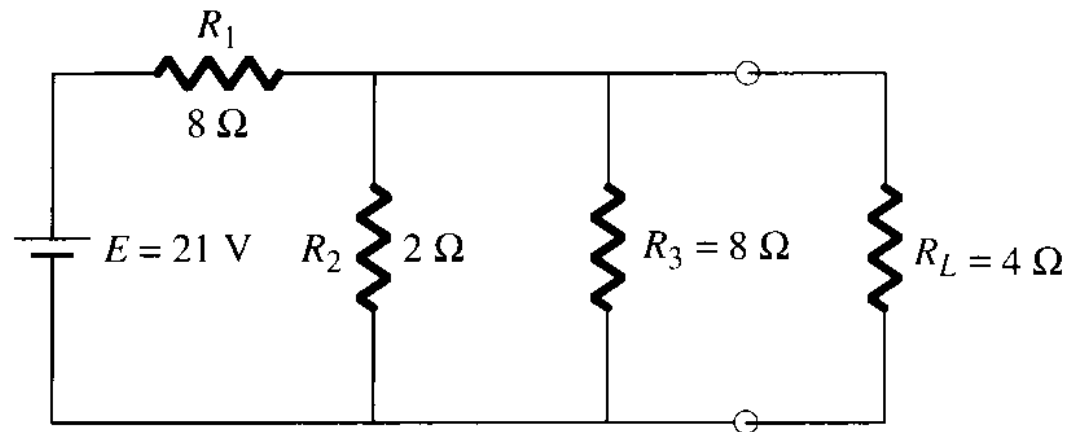


FIG. 3.89

# $R_{TH}$

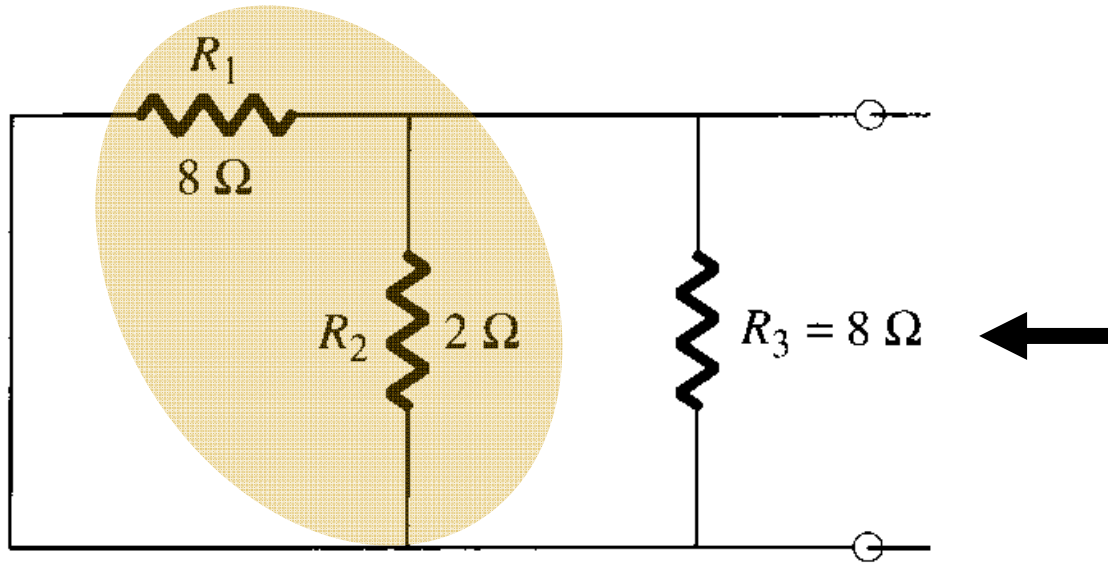


$$R_{TH} = (R_1 // R_2) // R_3 = 1.333\Omega$$

$E_{TH}$

$$R_T = (R_3 // R_2) + R_1 = 9.6\Omega$$

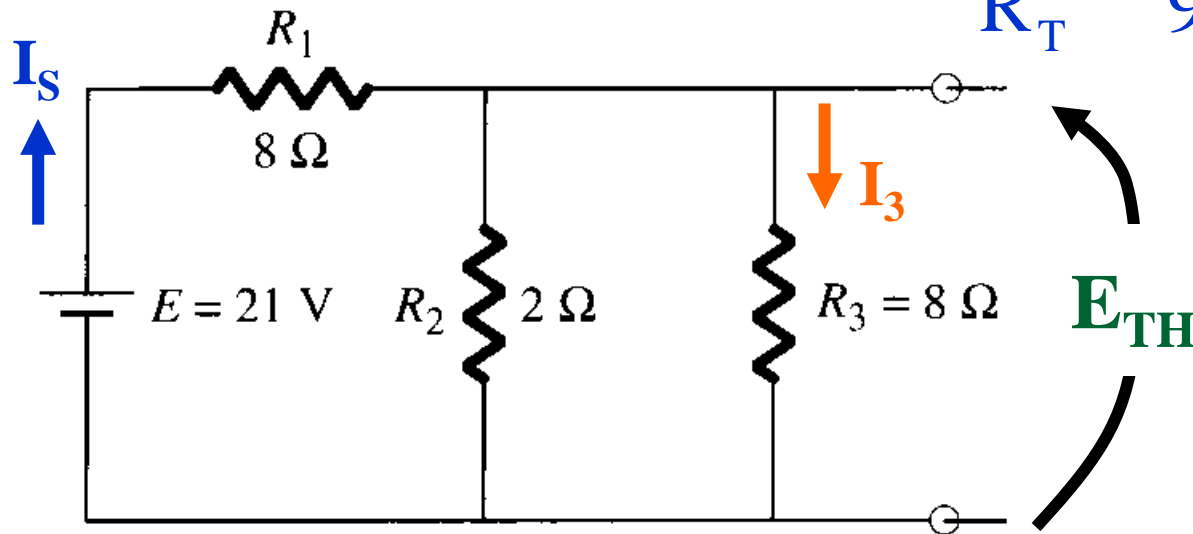
$$I_s = \frac{E}{R_T} = \frac{21V}{9.6\Omega} = 2.1985A$$



$$I_3 = I_s \times \frac{R_2}{R_2 + R_3} = 0.4375A$$

$$E_{TH} = I_3 \times R_3 = 3.5V$$

# Thévenin Network

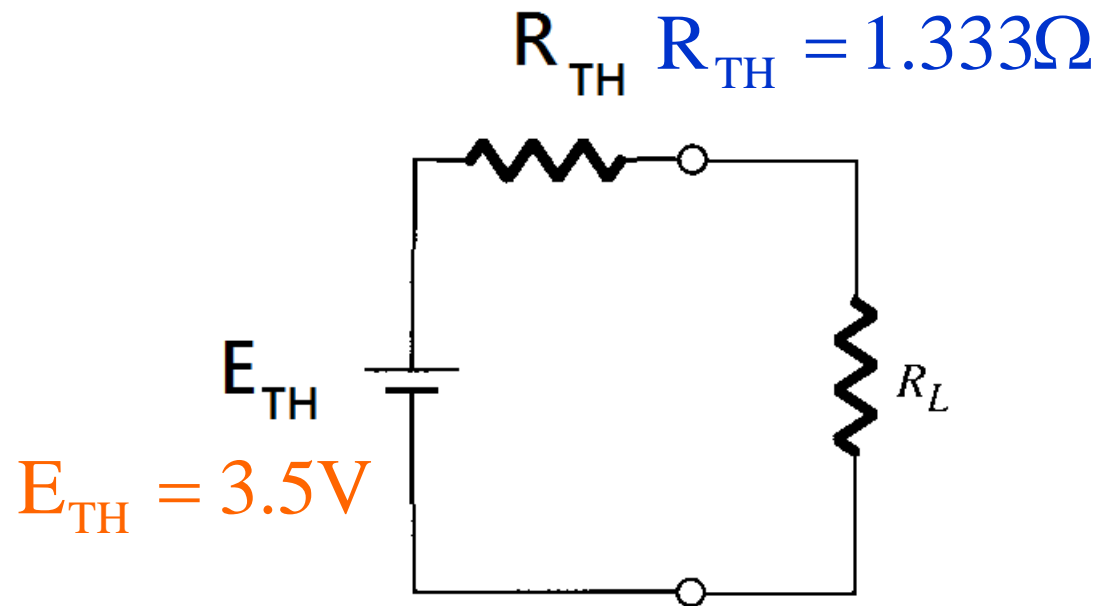

$$I_L = \frac{E_{TH}}{R_{TH} + R_L} = \frac{3.5V}{(1.333\Omega + 4\Omega)} = 0.656A$$

$$P = I_L^2 \times R_L = 1.721W$$

# Exercise 21 Thevenin network

21. a. Determine the value of  $R_L$  in Fig. 3.89 that would result in maximum power to  $R_L$ .
- b. Calculate the maximum power that could be delivered to  $R_L$  if it were changed to that value.
- c. Find the power delivered to  $R_L$  if  $R_L = 4 \Omega$  and verify that it is less than the maximum value in part (b).

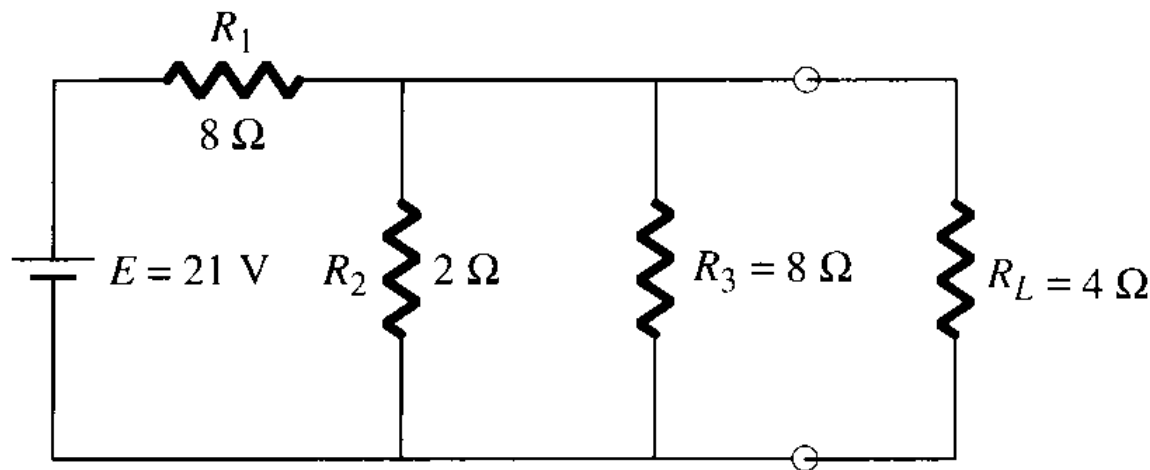


FIG. 3.89

# Solution

當  $R_L = R_{TH} = 1.333\Omega$

$$I_L = \frac{E_{TH}}{R_{TH} + R_L} = \frac{3.5V}{(1.333\Omega + 1.333\Omega)} = 1.3125A$$

$$P = I_L^2 \times R_L = 2.297W = \frac{E_{TH}^2}{4R_L} = \frac{E_{TH}^2}{4R_{TH}} = 2.297W$$

$$I_L = \frac{E_{TH}}{R_{TH} + R_L} = \frac{3.5V}{(1.333\Omega + 4\Omega)} = 0.656A$$

$$P = I_L^2 \times R_L = 1.721W \quad (\text{非最大})$$



# Exercise 22 Thevenin network

22. a. Find the Thévenin network for the network external to the resistor  $R_L$  in Fig. 3.90.  
b. Find  $R_L$  for maximum power to  $R_L$ .  
c. Find the maximum power to  $R_L$ .



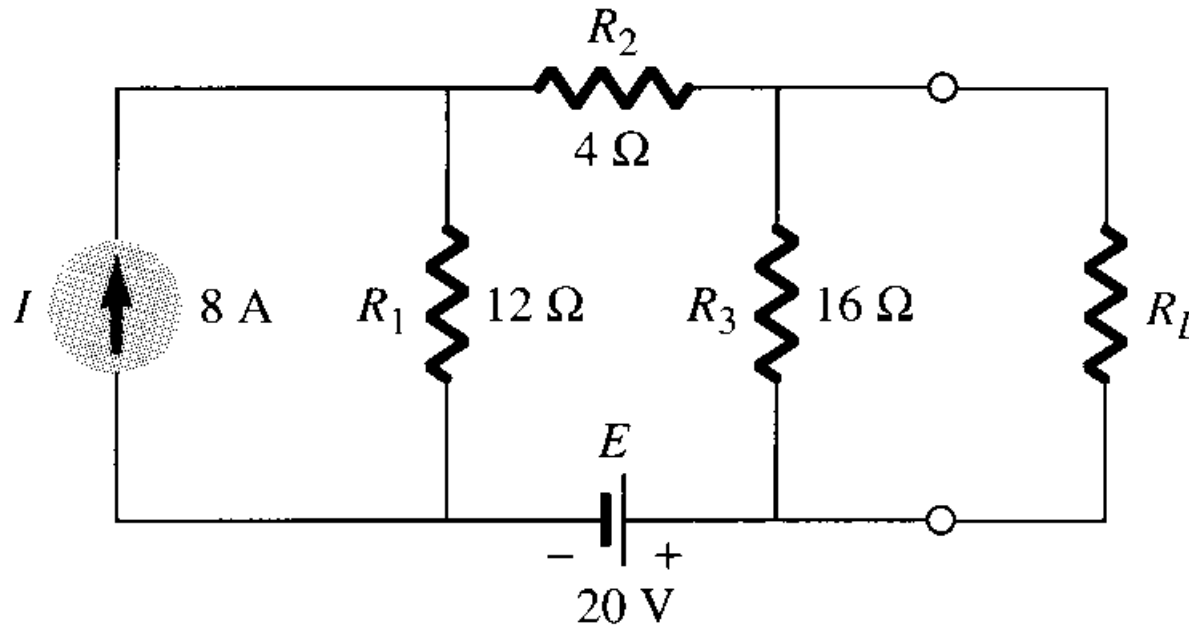



FIG. 3.90

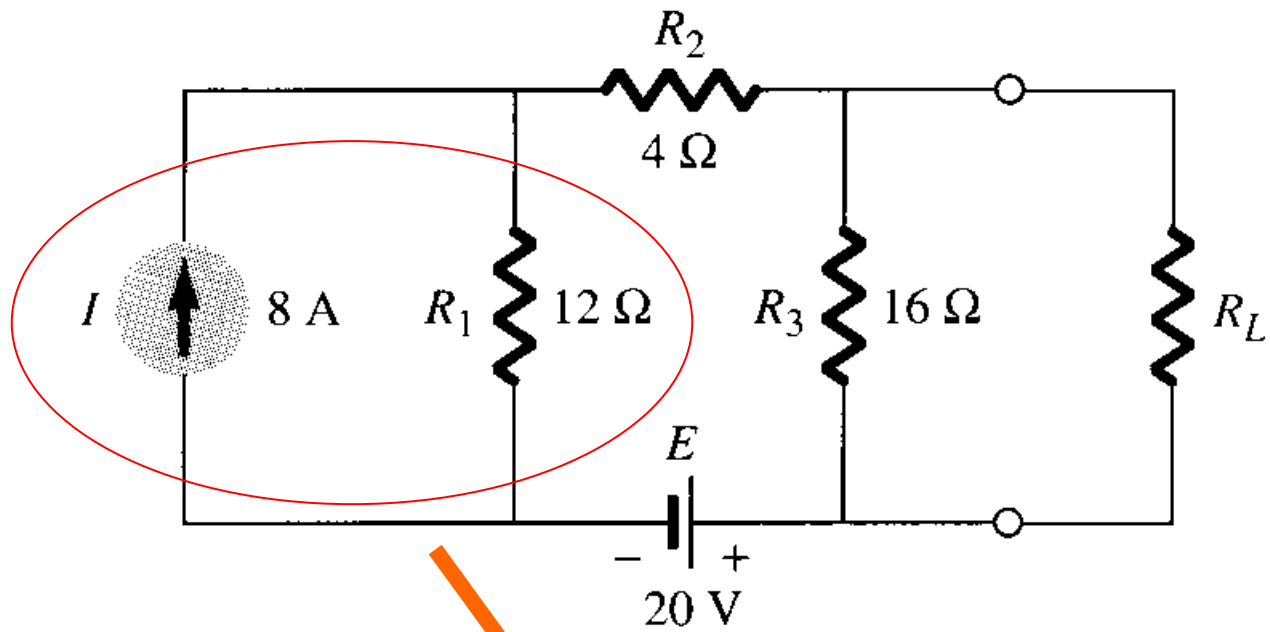

關鍵步驟

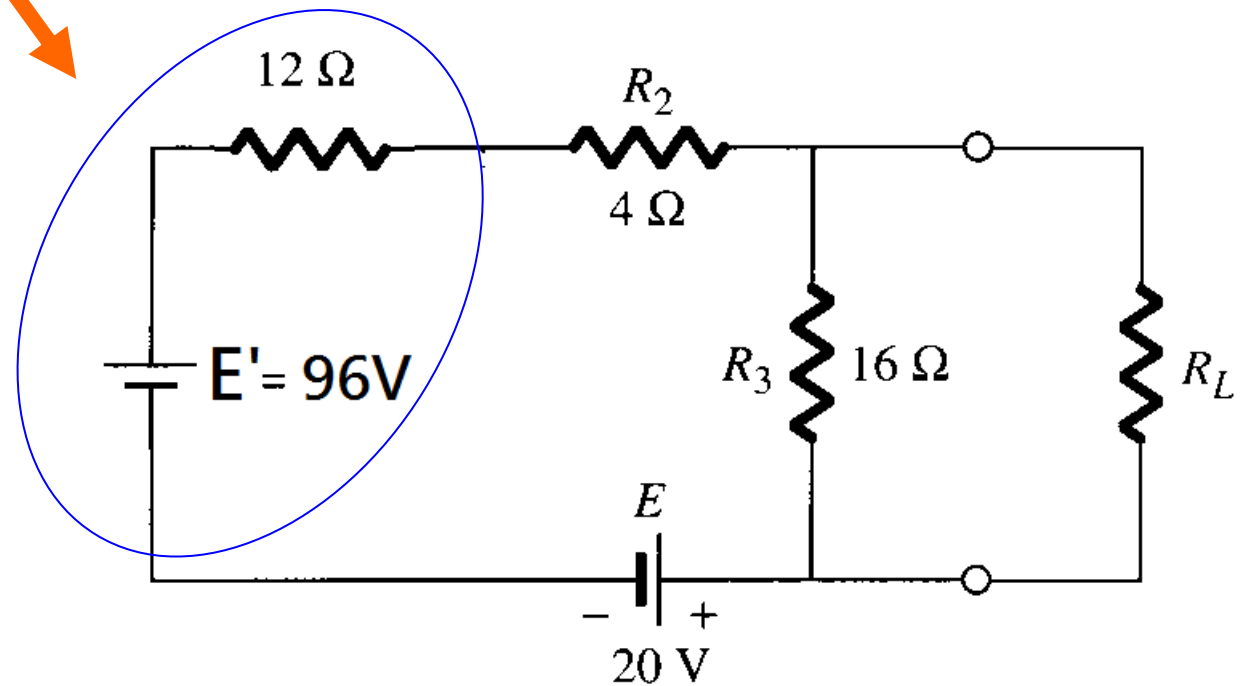


$R_{TH}$

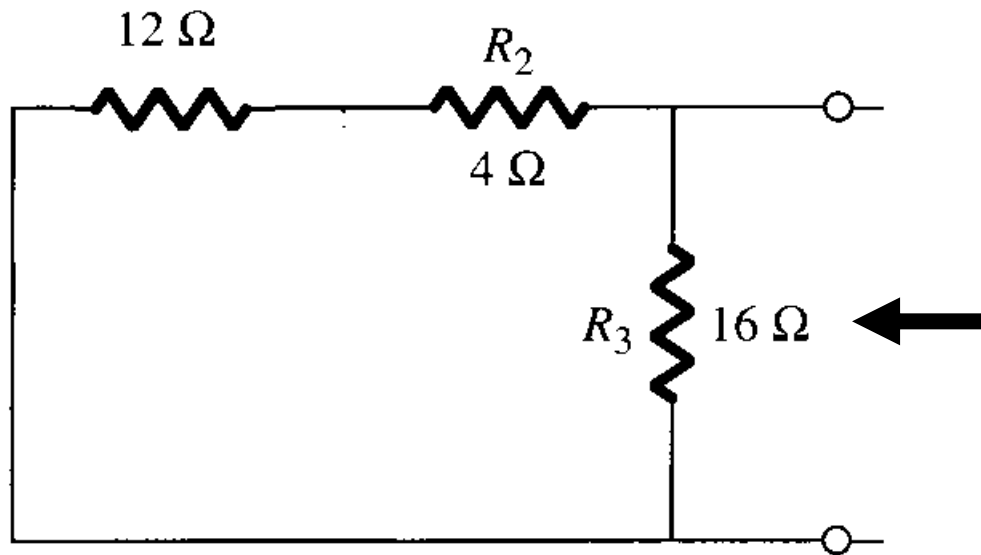


$$R_{TH} = (12\ \Omega + R_2) // R_3 = 8\ \Omega$$

# $E_{TH}$

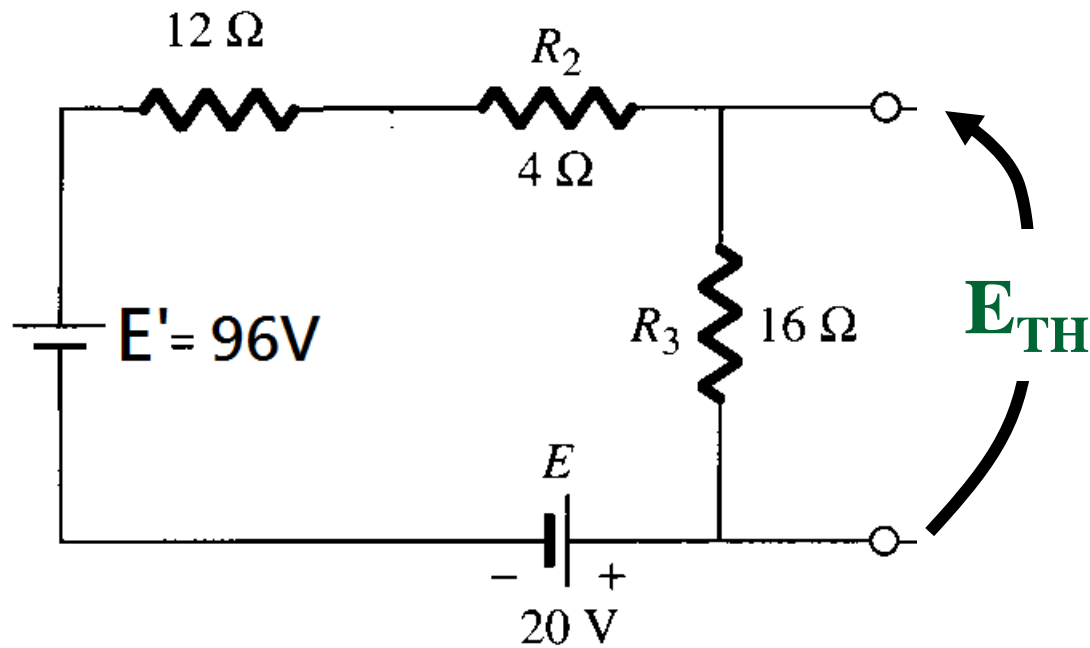

$$E_{TH} = (E' - E) \times \frac{R_3}{12\Omega + R_2 + R_3} = 38V$$

# Thévenin Network

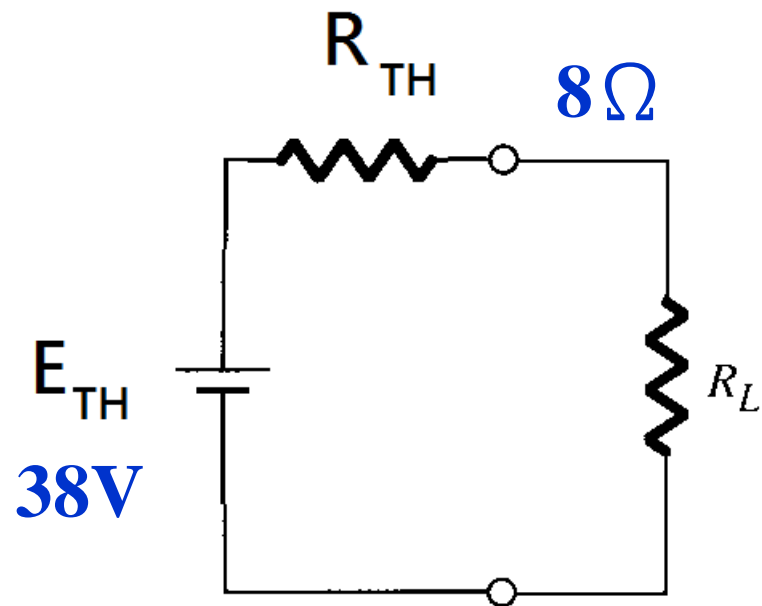

當  $R_L = R_{TH} = 8\Omega$

$$P_{\max} = \frac{E_{TH}^2}{4R_L} = \frac{E_{TH}^2}{4R_{TH}} = 45.125\text{W}$$