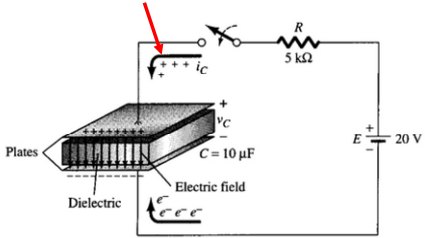
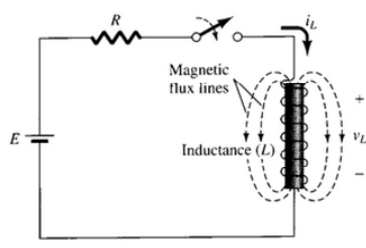
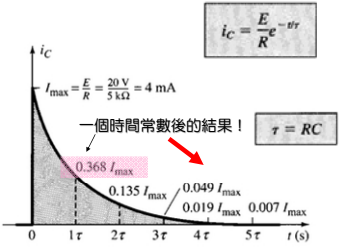
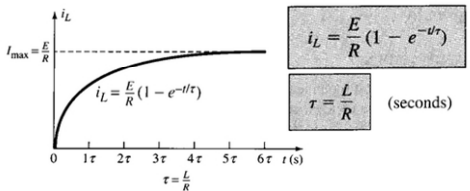
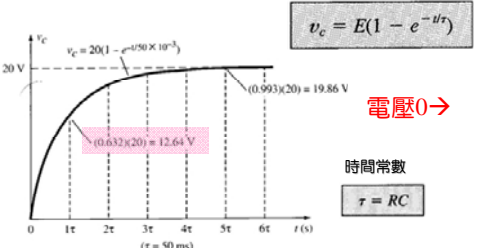
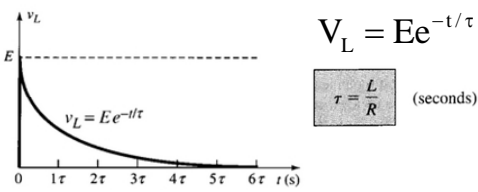
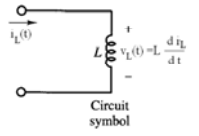


|   |   |
|---|---|
| <h3 style="text-align: center;">Charging &amp; Discharging 1/3</h3> <p style="color: red;">電流是變動的，不再用大寫的 I</p>   | <h3 style="text-align: center;">Charging &amp; Discharging 1/3</h3>   |
| <h3 style="text-align: center;">Charging &amp; Discharging 2/3</h3>  <p style="text-align: center;"><math>i_C = \frac{E}{R} e^{-t/\tau}</math>    電流 <math>\rightarrow 0</math></p> <p style="text-align: center;">一個時間常數後的結果！    <math>\tau = RC</math></p> <p style="color: red;">i<sub>C</sub>由E/R降低到零；<br/>V<sub>C</sub>由零充電上升到E時，電容器如同open circuit！</p>   | <h3 style="text-align: center;">Charging &amp; Discharging 2/3</h3> <p>□ 流經coil的電流i<sub>L</sub>，與電容器的v<sub>C</sub>相似。電流i<sub>L</sub>由零遞增到E/R。</p>  <p style="text-align: center;"><math>i_L = \frac{E}{R} (1 - e^{-t/\tau})</math>    <math>\tau = \frac{L}{R}</math> (seconds)</p>   |
| <h3 style="text-align: center;">Charging &amp; Discharging 3/3</h3>  <p style="text-align: center;"><math>v_C = E(1 - e^{-t/\tau})</math>    電壓 <math>0 \rightarrow</math></p> <p style="text-align: center;">時間常數    <math>\tau = RC</math></p>   | <h3 style="text-align: center;">Charging &amp; Discharging 3/3</h3> <p>□ 跨越coil的電壓v<sub>L</sub>，與電容器的i<sub>C</sub>相似。電壓v<sub>L</sub>由E降低到零。</p>  <p style="text-align: center;"><math>v_L = E e^{-t/\tau}</math>    <math>\tau = \frac{L}{R}</math> (seconds)</p>   |
| <h3 style="text-align: center;">v- i Relationship 1/2</h3> <p style="color: blue;">前面講的電壓是DC，一旦外加電壓是變動時...</p> <p>□ If the external voltage applied to the capacitor plates changes in time:</p> <p style="color: blue;"><math>q(t) = cv(t)</math> A time-varying voltage will cause charge to vary in time.</p> <p>□ Recalling the definition of current:</p> <p style="color: blue;"><math>i(t) = \frac{dq(t)}{dt} \Rightarrow i(t) = C \frac{dv(t)}{dt}</math> which is called <b>CIRCUIT LAW for a CAPACITOR.</b></p> | <h3 style="text-align: center;">v- i Relationship 1/2</h3> <p>□ 電感的電壓大小為電感量與電流變動率的乘積，此為電感的「歐姆定律」：</p> <p style="color: blue;"><math>v_L(t) = L \frac{di_L}{dt}</math></p>  <p style="text-align: center;">Circuit symbol</p> <p>L is called the inductance of the coil (電感)；<br/>電感的單位 H = V s/A；<br/>v<sub>L</sub>=感應電壓；L = 電感量；di<sub>L</sub>/dt=電流變動率</p> |

### v- i Relationship <sup>2/2</sup>

□ The voltage across a capacitor:

$$v_c(t) = \frac{1}{C} \int_{-\infty}^t i_c(t') dt'$$

□ The capacitor voltage depends on the past current through the capacitor, up until the present time, t.

$$v_o = v_c(t = t_o) = \frac{1}{C} \int_{-\infty}^{t_o} i_c(t') dt'$$

$$v_c(t) = \frac{1}{C} \int_{t_o}^t i_c(t') dt' + v_o \quad t \geq t_o$$

where  $v_o$  is sufficient to account for the entire past history of the capacitor current.

### v- i Relationship <sup>2/2</sup>

□ The current through an inductor:

$$i_L(t) = \frac{1}{L} \int_{-\infty}^t v_L(t') dt'$$

□ The inductor current depends on the past voltage across the inductor, up until the present time, t.

$$I_o = i_L(t = t_o) = \frac{1}{L} \int_{-\infty}^{t_o} v_L(t') dt'$$

$$i_L(t) = \frac{1}{L} \int_{t_o}^t v_L(t') dt' + i_o \quad t \geq t_o$$

where  $i_o$  is sufficient to account for the entire past history of the inductor voltage.

### Capacitor $v_c \rightarrow i_c$

$$i_c = C \frac{dv_c}{dt} \approx C \frac{\Delta v_c}{\Delta t}$$

0 → 2ms

$$i_c = (2\mu F) \frac{8V}{2ms} = +8mA$$

2 → 5ms


$$i_c = (2\mu F) \frac{-16V}{3ms} = -10.67mA$$

5 → 8ms

$$i_c = (2\mu F) \frac{12V}{3ms} = +8mA$$

8 → 10ms
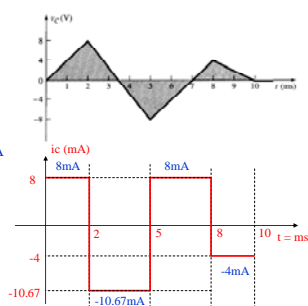
$$i_c = (2\mu F) \frac{-4V}{2ms} = -4mA$$



### Inductor $i_L \rightarrow v_L$

$$v_L = L \frac{di_L}{dt} \approx L \frac{\Delta i_L}{\Delta t}$$

0 → 3ms

$$v_L = 0V$$

3 → 7ms


$$v_L = (0.5H) \frac{10\mu A}{4ms} = 1.25mV$$

7 → 12ms


$$v_L = (0.5H) \frac{5\mu A}{5ms} = 0.5mV$$

12 →


$$v_L = 0V$$

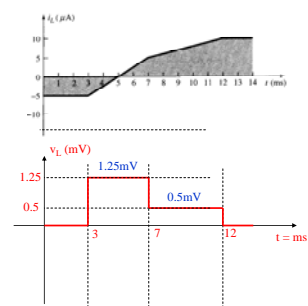

### 電容器串、並聯

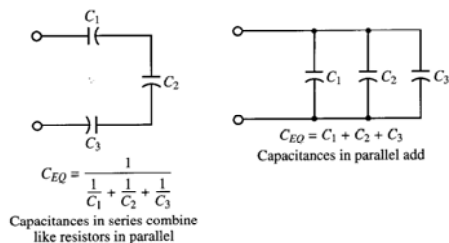

### 電感串、並聯

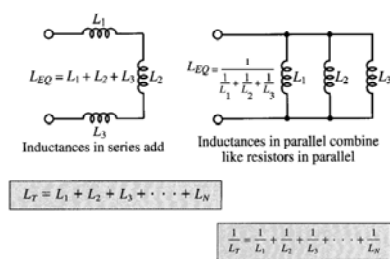

### Energy Storage in Capacitor

□ The energy stored in the capacitor,  $W_c(t)$

$$W_c(t) = \int P_c(t') dt' = \int v_c(t') i_c(t') dt' = \int v_c(t') C \frac{dv_c(t')}{dt'} dt'$$

$$W_c(t) = \frac{1}{2} C v_c^2(t)$$

### Energy Storage in Inductor

□ The energy stored in the inductor,  $W_L(t)$

$$P_L(t) = i_L(t) v_L(t) = i_L(t) L \frac{di_L(t)}{dt} = \frac{d}{dt} \left[ \frac{1}{2} L i_L^2(t) \right]$$

$$W_L(t) = \int P_L(t') dt' = \int v_L(t') i_L(t') dt' = \int i_L(t') L \frac{di_L(t')}{dt'} dt'$$

$$W_L(t) = \frac{1}{2} L i_L^2(t)$$

### 電容的正弦響應 1/2

$i_c(t) = C \frac{dv_c(t)}{dt}$       $v_L(t) = L \frac{di_L}{dt}$

□ 假設有一正弦電流通過一個電容，則電容的電壓響應方程式為？

$i = C \frac{dv}{dt}$       $v = V_{peak} \sin \omega t$

$= C \frac{d}{dt} V_{peak} \sin \omega t$


$= \omega C V_{peak} \cos \omega t$

$= I_{peak} \cos \omega t$

$= I_{peak} \sin(\omega t + 90^\circ)$

$I_{peak} = \omega C V_{peak} = \frac{V_{peak}}{X_C}$

$X_C = \frac{1}{2\pi f C}$

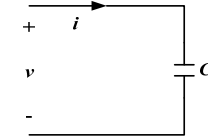

50

### 電感的正弦響應 1/2

$i_c(t) = C \frac{dv_c(t)}{dt}$       $v_L(t) = L \frac{di_L}{dt}$

□ 假設有一正弦電流通過一個電感，則電感的電壓響應方程式為？

$v = L \frac{di}{dt}$       $i = I_{peak} \sin \omega t$

$= L \frac{d}{dt} I_{peak} \sin \omega t$


$= \omega L I_{peak} \cos \omega t$

$= V_{peak} \cos \omega t$

$= V_{peak} \sin(\omega t + 90^\circ)$

$V_{peak} = \omega L I_{peak} = X_L I_{peak}$


$X_L = \omega L = 2\pi f L$

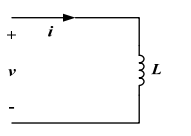

44

### 電容的正弦響應 2/2

修正

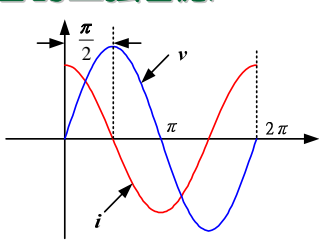


電壓與電流間有相位差，流經電感的電流，比跨越電感的電壓，領先90°。或者說，電壓落後電流90°。

51

### 電感的正弦響應 2/2

修正

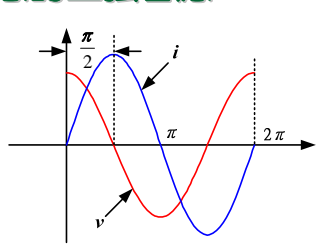

電壓與電流間有相位差，流經電感的電流，比跨越電感的電壓，落後90°。或者說，電壓領先電流90°。

45

### Capacitor C 1/3


□ 當sinusoidal voltage跨越電容時，電壓、電流與電容的關係如何？

電壓與電流間有相位差，流經電感的電流，比跨越電感的電壓，領先90°。或者說，電壓落後電流90°。

$e = 10 \sin 377t$   
 $f = 60 \text{ Hz}$

$X_C = \frac{1}{\omega C} = \frac{1}{(377)(10 \times 10^{-6})}$   
 $= \frac{10^6}{3770} = 265.25 \Omega$   
 $i = 37.7 \times 10^{-3} \sin(377t + 90^\circ)$   
 $10 \div 265.25 = 0.0377$

$i = 37.7 \text{ mA}$

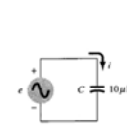

52

### Inductor L 1/3


□ 當sinusoidal voltage跨越電感時，電壓、電流與電感的關係如何？

電壓與電流間有相位差，流經電感的電流，比跨越電感的電壓，落後90°。或者說，電壓領先電流90°。

$e = 20 \sin 377t$   
 $f = 60 \text{ Hz}$

$X_L = \omega L = (377)(0.5) = 188.5 \Omega$   
 and  
 $i = 106.1 \times 10^{-3} \sin(377t - 90^\circ)$   
 $20 \div 188.5 = 0.1061$

$i = 106.1 \text{ mA}$

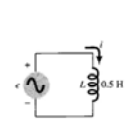

46

### Capacitor C 2/3

電壓的peak value與電流的peak value關係

$I_{peak} = \frac{V_{peak}}{X_C}$

其中， $X_C$ 稱為電容的電抗 (reactance)，單位為Ohms。電容的電抗就像電阻 (器) 的電阻一樣，用來限制電流的流動。

$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$  (ohms)

53

### Inductor L 2/3

電壓的peak value與電流的peak value關係

$I_{peak} = \frac{V_{peak}}{X_L}$

其中， $X_L$ 稱為電感的電抗 (reactance)，單位為Ohms。電感的電抗就像電阻 (器) 的電阻一樣，用來限制電流的流動。

$X_L = \omega L = 2\pi f L$

47

### Capacitor C 3/3

❑ 電容對於AC signal的反應與電阻不一樣。電容不像電阻消耗功率，而是將電能分別以電場的型態儲存起來，且它們的reactance (電抗) 與頻率有關。

低頻時電容的電抗很大，就像open-circuit equivalent (斷路)

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C} \quad (\text{ohms})$$

頻率越高電抗越低，形同短路。

### Inductor L 3/3

❑ 電感對於AC signal的反應與電阻不一樣。電感不像電阻消耗功率，而是將電能分別以磁場的型態儲存起來，且它們的reactance (電抗) 與頻率有關。

$$X_L = \omega L = 2\pi f L$$

頻率越高電抗越大，形同斷路。

低頻時電感的電抗為零，就像short-circuit equivalent (短路)。

### Generalized Impedance

Time domain 寫法

$$v_s(t) = \sqrt{2}A \sin \omega t$$

AC circuits in phasor/impedance form

$$V_s(j\omega) = A e^{j\phi} = A \angle \phi$$

Z is the impedance of each circuit element

BLOCK IMPEDANCE

### Generalized Impedance

$$v_s(t) = \sqrt{2}A \sin \omega t \rightarrow V_s(j\omega) = A e^{j\phi} = A \angle \phi$$

Z is the impedance of each circuit element

BLOCK IMPEDANCE

AC circuits in phasor/impedance form

$$Z(j\omega) = \frac{V_s(j\omega)}{I(j\omega)}$$

### Capacitor 1/3

❑ Recalling the defining relationships for the ideal capacitor :

$$i_C(t) = C \frac{dv_C(t)}{dt} \quad v_C(t) = \frac{1}{C} \int i_C(t') dt'$$

❑ Let  $v_C(t) = v_s(t)$  and  $i_C(t) = i_s(t)$ , then the following expression may be derived for the capacitor current :

$$i_C(t) = C \frac{dv_C(t)}{dt} = C \frac{d}{dt} (\sqrt{2}A \sin \omega t)$$

$$= C(\sqrt{2}A\omega \cos \omega t) = \omega C \sqrt{2}A \sin(\omega t + \frac{\pi}{2})$$

### Inductor 1/3

❑ Recalling the defining relationships for the ideal inductor :

$$v_L(t) = L \frac{di_L(t)}{dt} \quad i_L(t) = \frac{1}{L} \int v_L(t') dt'$$

❑ Let  $v_L(t) = v_s(t)$  and  $i_L(t) = i_s(t)$ , then the following expression may be derived for the inductor current :

$$i_L(t) = \frac{1}{L} \int v_s(t') dt' = -\frac{\sqrt{2}A}{\omega L} \cos \omega t = \frac{1}{L} \int \sqrt{2}A \sin \omega t' dt'$$

$$= -\frac{\sqrt{2}A}{\omega L} \cos \omega t = \frac{\sqrt{2}A}{\omega t} \sin(\omega t - \frac{\pi}{2})$$

### Capacitor 2/3

❑ This result can be seen by writing the capacitor voltage and current in time-domain form :

$$v_C(t) = v_s(t) = \sqrt{2}A \sin(\omega t)$$

$$i(t) = i_C(t) = \omega C \sqrt{2}A \sin(\omega t + \frac{\pi}{2})$$

The capacitor current is shifted in phase by 90 with respect to the voltage. (電容電流與電壓的相位移為領先90°)

❑ 電容電流的大小不僅是電壓大小的scaled version而已，而是還depends on the frequency  $\omega$ ，甚至與電壓有相位落後！因為電容不是單純的電阻！

### Inductor 2/3

❑ This result can be seen by writing the inductor voltage and current in time-domain form :

$$v_L(t) = v_s(t) = \sqrt{2}A \sin(\omega t)$$

$$i(t) = i_L(t) = \frac{\sqrt{2}A}{\omega t} \sin(\omega t - \frac{\pi}{2})$$

The inductor current is shifted in phase by 90 with respect to the voltage. (電感電流與電壓的相位移為落後90°)

❑ 電感電流的大小不僅是電壓大小的scaled version而已，而是還depends on the frequency  $\omega$ ，甚至與電壓有相位落後！因為電感不是單純的電阻！

## Capacitor<sup>3/3</sup>

□ Using phasor notation :

$$V_s(j\omega) = A\angle 0 \quad I(j\omega) = \omega C A \angle \pi/2$$

□ The impedance of the capacitor is defined as

$$Z_C(j\omega) = \frac{V_s(j\omega)}{I(j\omega)} = \frac{1}{\omega C} \angle -\pi/2 = \frac{1}{j\omega C}$$

The impedance of the capacitor varying as an inverse function of frequency。在低頻時，電容的impedance很高，就像開路一般；相對的，在高頻時，電容的impedance很低，就像短路一般。

$$v(t) = \sqrt{2}A \sin(\omega t + \phi) \Leftrightarrow V(j\omega) = A e^{j\phi} = A\angle\phi$$

89

## Inductor<sup>3/3</sup>

□ Using phasor notation :

$$V_s(j\omega) = A\angle 0 \quad I(j\omega) = \frac{A}{\omega L} \angle -\pi/2$$

□ The impedance of the inductor is defined as

$$Z_L(j\omega) = \frac{V_s(j\omega)}{I(j\omega)} = \omega L \angle \pi/2 = j\omega L$$

Impedance與  
頻率成正比

An inductor will IMPEDE current flow in proportional to the sinusoidal frequency of the source signal。在低頻時，電感的impedance很低，就像短路一般；相對的，在高頻時，電感的impedance很高，就像開路一般。

$$v(t) = \sqrt{2}A \sin(\omega t + \phi) \Leftrightarrow V(j\omega) = A e^{j\phi} = A\angle\phi$$

86