

**Equations:**

$$I = \frac{Q}{t} \text{ (A)}$$

$$V = \frac{W}{Q} \text{ (V)}$$

$$I = \frac{E}{R} \text{ (A)}$$

$$R = \rho \frac{\ell}{A} \text{ (\Omega)}$$

$$\frac{T + t_1}{R_1} = \frac{T + t_2}{R_2}$$

$$P = EI = VI = I^2R = \frac{V^2}{R}$$

$$W = Pt \text{ (J, W/s)}$$

$$\text{kwh} = \frac{Pt}{1000}$$

$$1 \text{ hp} = 746 \text{ W}$$

**Series Circuits:**

$$R_T = R_1 + R_2 + R_3 + \dots + R_N; R_T = NR$$

$$E = V_1 + V_2 + V_3 + \dots + V_N$$

$$I = \frac{E}{R_T}$$

$$P_T = EI = I^2R_1 + I^2R_2 + \dots + I^2R_N$$

$$V_x = \frac{R_x E}{R_T}$$

**Parallel Circuits:**

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_N}; R_T = \frac{R}{N}$$

$$R_T = \frac{R_1 R_2}{R_1 + R_2}$$

$$I_T = \frac{E}{R_T}$$

$$I_T = I_1 + I_2 + I_3 + \dots + I_N$$

$$I_1 = \frac{R_2 I_T}{R_1 + R_2}, I_2 = \frac{R_1 I_T}{R_1 + R_2}$$

**PROBLEMS**

**SECTION 2.2 Current**

1. If  $24 \times 10^{16}$  electrons pass through a conductor in  $\frac{1}{2}$  min, determine:

a. Charge in coulombs.  $24 \times 10^{16} \text{ electrons} \times \frac{1.6 \times 10^{-19} \text{ Coulomb}}{1 \text{ electron}} = 38.45 \times 10^{-3} \text{ C}$

b. Current.

b. Current =  $\frac{Q}{t} = \frac{38.45 \times 10^{-3} \text{ C}}{30 \text{ s}} = 1.282 \text{ mA}$

3. Charge  $Q = It = (16 \mu A)(10s) = 160 \mu C$

7 (b)  $0.01 ft = 0.12 in = 120 mils$   
 $A_{cm} = (d_{mils})^2 = (120 mils)^2 = 14,400 CM$

(c)  $0.1 cm = 0.03937 in = 39.37 mils$   
 $A_{cm} = (39.37 mils)^2 = 1550 CM$

9.  $40mC$  电荷跨越  $120V$  电压差, energy?  
 $V = \frac{W}{Q} \rightarrow W = VQ = (120V)(40 \times 10^{-3} C) = 4.8 \text{ joules}$

11.  $18 \times 10^{18}$  电子跨越  $12V$ , energy?  
 $18 \times 10^{18}$  电子相当於多少  $Q$ ?  
 $Q = 18 \times 10^{18} \text{ electrons} \times \frac{1.6 \times 10^{-19} C}{\text{electron}} = 2.88 C$   
 $W = V \times Q = (12V)(2.88 C) = 34.6 J$

13. Ohm's Law  $R = \frac{E}{I} = \frac{1.5V}{1.8mA} = 833.33 \Omega$   
 Note: 电压差  $E$

2. How long will it take 1600 mC to pass through a copper conductor if the current is 0.5 A?

3. How much charge has passed through a conductor if the current is 16  $\mu A$  for 10 s?  $Q = It$

4. For a current of 1 mA, how many electrons will pass a particular point in the circuit in 1 s? Write the number out in full decimal form (all the zeros). Is it a significant number for such a small current level?

5. Write the following quantities in the most convenient form using the prefixes in Table 2.1.

- a. 0.050 A  $50 mA$
- b. 0.0004 V  $0.4 mV$
- c.  $3 \times 10^4$  V  $30 kV$
- d. 1200 V  $1.2 kV$
- e. 0.0000007 A  $0.7 \mu A$
- f. 32,000,000 V  $32 MV$

6. What is the resistance of 1000 ft of No. 12 house wire?

7. What is the area in circular mils of wires having the following diameters?

- a.  $\frac{1}{32}$  in.  $a. \frac{1}{32} in = 0.03125 in = 31.25 mils$   
 $A_{cm} = (d_{mils})^2 = (31.25 mils)^2 = 976.56 CM$
- b. 0.01 ft
- c. 0.1 cm

8. What is the diameter in inches of wires having the following areas in circular mils?

- a. 10,000 CM
- b. 625 CM
- c. 50,000 CM

SECTION 2.3 Voltage

9. Determine the energy expended (in joules) to bring a charge of 40 mC through a potential difference of 120 V.

10. What is the potential difference between two points in an electric circuit if 200 mJ of energy is required to bring a charge of 40  $\mu C$  from one point to the other?

11. How much energy is required to move  $18 \times 10^{18}$  electrons through a potential difference of 12 V?

12. How much energy is expended to maintain a current of 10 mA between two points in an electric circuit for 5 s if the potential difference between the two points is 20 mV?

SECTION 2.5 Resistance and Ohm's Law

13. Determine the internal resistance of a battery-operated clock if a current of 1.8 mA results from an applied voltage of 1.5 V. 求 battery 的内部电阻

14. Determine the current through a soldering iron if 120 V is applied. The iron has a resistance of 18  $\Omega$ .

15. Find the voltage drop across a 2.2-M $\Omega$  resistor with a current of 30  $\mu A$  passing through it. What resistance would be required to limit the current to 1.5 A if the applied voltage is 64 V? 跨越 2.2M $\Omega$  的电阻的电压降

$V = RI = (2.2 M\Omega)(30 \mu A) = 66 V$   
 施予电压 64V, 限制电流 1.5A, 电阻?  
 $R = \frac{V}{I} = \frac{64 V}{1.5 A} = 42.67 \Omega$

16. Determine the resistance of 50 ft of  $\frac{1}{16}$ -in.-diameter copper wire.
17. Calculate the resistance of 600 ft of No. 14 wire using Table 2.2.
18. Determine the diameter (in inches) of a copper inductor having a length of 200 ft and a resistance of 0.2  $\Omega$ .
19. What is the resistance of 1 mi of No. 12 house wire? How does it compare with the resistance of 1 k $\Omega$  connected to the end of the conductor?
20. If the resistance of a copper conductor is 2  $\Omega$  at room temperature ( $T = 20^\circ\text{C}$ ), what is its resistance at 100 $^\circ\text{C}$  (the boiling point of water)?

#14 每 1000ft, 2.525  $\Omega$   
 因此, 600ft 的 wire, 电阻  $600\text{ft} \times \frac{2.525\Omega}{1000\text{ft}} = 1.515\Omega$

21. At what temperature will the resistance of a No. 8 copper wire double if its resistance at  $T = 20^\circ\text{C}$  is 1  $\Omega$ ?
22. If the resistance of a copper conductor 400 ft long is 10  $\Omega$  at room temp. ( $T = 20^\circ\text{C}$ ), what is its resistance at  $-20^\circ\text{C}$ .

#12. 每 1000ft, 1.588  $\Omega$   
 因此, 1 mi = 5,280ft 的 wire, 电阻:  
 $5,280\text{ft} \times \frac{1.588\Omega}{1,000\text{ft}} = 8.38\Omega < 1\text{ k}\Omega$

23. a. Determine the resistance of a molded composition resistor with the following color bands: first: red; second: red; (third) brown; fourth: gold.
- b. Indicate its expected range of values.

#8  $t_1 = 20^\circ\text{C}$  为 1  $\Omega$ ,  $t_2 = ?$  为 2  $\Omega$   
 Copper 电阻与温度  $T = -234.5^\circ\text{C}$   
 $\frac{T+t_1}{R_1} = \frac{T+t_2}{R_2} \quad \frac{20+20}{1\Omega} = \frac{20+t_2}{2\Omega}$

24. Determine the color bands of a 100-k $\Omega$  resistor with a tolerance of 5%.
25. Determine the color bands of a 3.952 resistor with a tolerance of 10%.

red: 2, brown 10<sup>1</sup>, gold  $\pm 5\%$   
 $t_2 = 20^\circ\text{C}$   
 23.  $22\Omega \times 10^1 \pm 5\%$   
 $209\Omega \sim 231\Omega$

25. 橙, 白, 金, 银 Orange, white, Gold, Silver

**SECTION 2.6 Power, Energy, Efficiency**

26. Determine the power delivered by a 12-V battery at a current drain of 240 mA.
27. Calculate the power dissipated by a 2.2-k $\Omega$  resistor having a current of 4 mA passing through it.
28. A 280-W television set is connected to a 120-V outlet. Determine the current drawn by the set.
29. Determine the total energy dissipated by a 1400-W toaster used for 3.5 min.
30. Calculate the cost of using the following appliances for the indicated time period if the unit cost is 9 cents/kWh.
  - a. Six 60-W bulbs for 6 h.
  - b. 8-W clock for 30 days (1 month).
  - c. 160-W television set for 4 h 30 min.
  - d. 5000-W clothes dryer for 45 min.

Power =  $I^2 R = (4\text{mA})^2 (2.2\text{k}\Omega) = 35.2\text{ mW}$

$W = Pt = (1400\text{W})(210\text{s}) = 294\text{ kJ}$

下列设备耗能量 =  $6 \times 60\text{W} \times 6\text{h} + 8\text{W} \times 24\text{h/d} \times 30\text{d} + 160\text{W} \times 4.5\text{h} + 5000\text{W} \times \frac{3}{4}\text{h}$

31. Determine the cost of using an 8-W night light for 1 year (365 days) if the cost is 9 cents/kWh.
32. How long can we use a welding unit for \$1.00 if the unit draws 14 A at 220 V and the cost is 9 cents/kWh?
33. Determine the applied power of a system that has an output power of 320 W and an efficiency of 86%.
34. a. A 2.2-hp motor has an input power demand of 2400 W. Determine its efficiency.  
 b. If the applied voltage is 120 V, find the input current.  
 c. What is the power lost in the energy transfer (in watts)?

(31) 1 year = 365 days = 8760 h  
 消耗能量  $W = \frac{Pt}{1000} = \frac{8\text{W} \times 8760\text{h}}{1000} = 70.08\text{ kWh}$   
 Cost =  $W \times 9\text{ cents/kWh} = (70.08\text{ kWh}) \times (9\text{ cents/kWh}) = 630.72\text{¢}$

(33)  $\eta = 86\%$   
 $\eta = \frac{P_o}{P_i} \rightarrow P_i = \frac{P_o}{\eta} = \frac{320\text{W}}{0.86} = 372.09\text{ W}$

(a) Output Power  $P_o = 2.2\text{ hp} = 2.2\text{ hp} \times 746\text{ W/hp}$

$\eta = \frac{P_o}{P_i} = \frac{1641.2\text{W}}{2400\text{W}} = 68.4\%$

(b)  $P_i = 2400\text{W} = E \times I = (120\text{V}) \times I \rightarrow I = \frac{2400\text{W}}{120\text{V}} = 20\text{ A}$

(c) Power loss =  $P_i - P_o = 758.8\text{ W}$

(a) 有3個 System 連接, total efficiency

$$\eta_T = \eta^3 = (0.9)^3 = 72.9\%$$

(b) 2個  $\eta = 90\%$  的系統與1個  $\eta = 20\%$  的系統連接

$$\eta_T = (0.9)^2 (0.2) = 16.2\%$$

35. The total efficiency of systems in cascade (one following the other) is the product of the individual efficiencies. With this in mind:
- What is the total efficiency of three systems in cascade with efficiencies of 90% each?
  - What is the total efficiency of three systems in cascade if two have an efficiency of 90% and one has an efficiency of 20%?
  - What conclusions can you draw from the results for parts (a) and (b)?

**SECTION 2.8 Series Dc Networks**

36. Find the total resistance of the networks in Fig. 2.55.


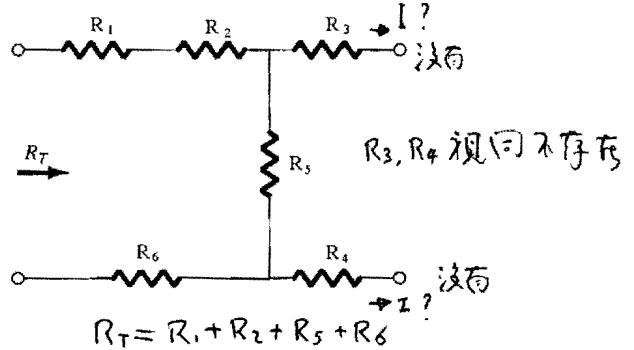
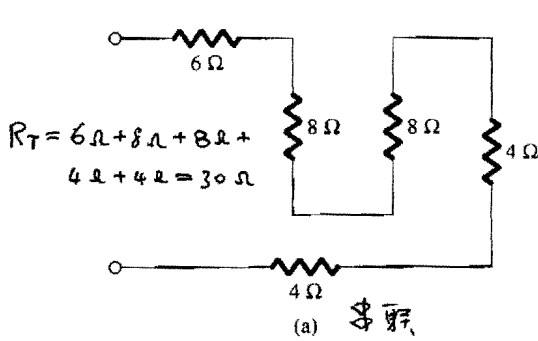
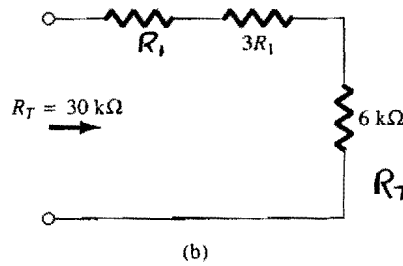


FIG. 2.55

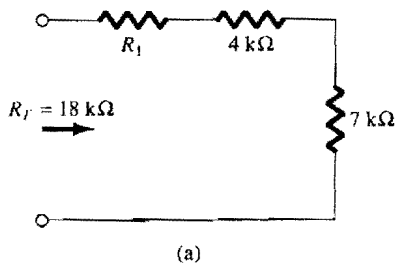37. Determine  $R_1$  for the networks in Fig. 2.56.



$$R_T = 18k\Omega = R_1 + 4k\Omega + 7k\Omega$$

$$R_1 = 7k\Omega$$

$$R_T = R_1 + 3R_1 + 6k\Omega = 30k\Omega$$

$$R_1 = 6k\Omega$$

FIG. 2.56

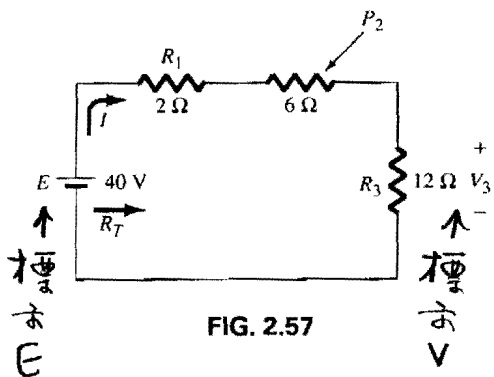


FIG. 2.57

38. For the circuit in Fig. 2.57, determine:

- $R_T$ .
- $I$ .
- $V_3$ .
- $P_2$ .

38.


- Total resistance  $R_T = 2\Omega + 6\Omega + 12\Omega = 20\Omega$
- 由電池流出來的電流  $I = \frac{E}{R_T} = \frac{40V}{20\Omega} = 2A$
- 流經串聯元件的電流都是 2A  
因此  $V_3 = I \times R_3 = (2A)(12\Omega) = 24V$
- 6Ω 電阻消耗的  $P_2$   
 $P_2 = I^2 \times 6\Omega = (2A)^2 (6\Omega) = 24W$

39. Determine the unknown quantities for the networks in Fig.

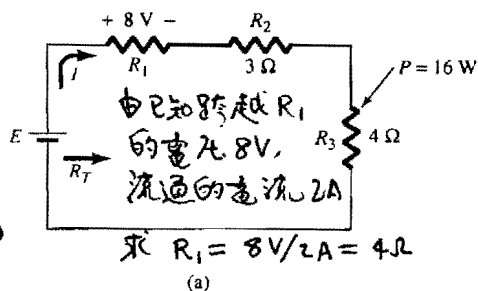
2.58. 由已知  $R_3$  的 Power 16W 与 电阻值  $4\Omega$ , 求 电流  $I$ ,  $P = I^2 R_3$ ,  $I = 2A$

$$R_T = R_1 + R_2 + R_3 = 11\Omega$$

$$E = I \times R_T = (2A)(11\Omega) = 22V$$



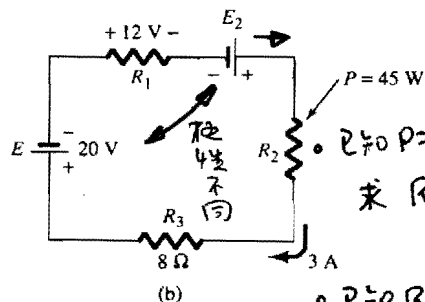由已知跨越  $R_1$  的电压 8V, 流通的电流 2A  
求  $R_1 = 8V/2A = 4\Omega$



已知  $P=45W$ ,  $I=3A$   
求  $R_2 = 5\Omega$

FIG. 2.58

由电流方向可判定  $E_2 > E$

已知  $R_1$  的电压降 12V, 流通电流  $I=3A$ , 求  $R_1 = 4\Omega$


$R_T = R_1 + R_2 + R_3 = 17\Omega$

$E_2 - 20V = R_T \times I$

若电流方向反过来

$\rightarrow 20V - E_2 = R_T \times I$

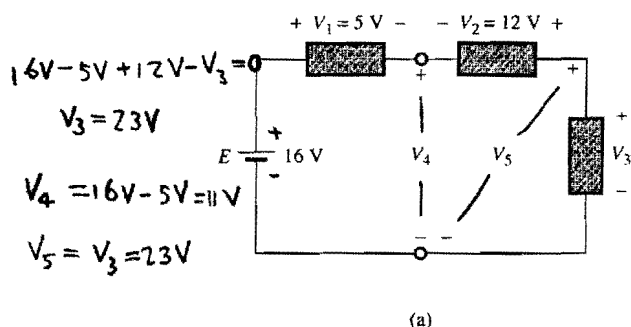40. Determine the unknown voltages for the circuits in Fig. 2.59 using Kirchhoff's voltage law.




$$16V - 5V + 12V - V_3 = 0$$

$$V_3 = 23V$$

$$V_4 = 16V - 5V = 11V$$

$$V_5 = V_3 = 23V$$

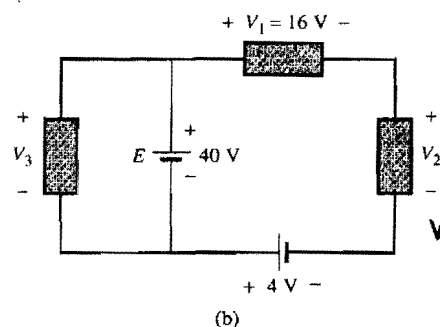

$$V_3 = E = 40V$$

$$E - 16V - V_2 + 4V = 0$$

$$V_2 = 28V$$

FIG. 2.59

41. Determine the voltages  $V_3$  and  $V_4$  using the voltage-divider rule for the network in Fig. 2.60.

利用 voltage-divider rule

$$V_3 = E \times \frac{R_3}{R_1 + R_2 + R_3}$$

$$V_4 = E \times \frac{R_2 + R_3}{R_1 + R_2 + R_3}$$

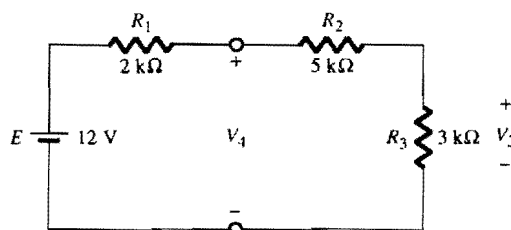


FIG. 2.60

42. Determine  $R_2$  for the given voltage level for the network in Fig. 2.61 using the voltage-divider rule.

$$V_2 = \frac{R_2}{R_1 + R_2} E \rightarrow R_2 = 6k\Omega$$

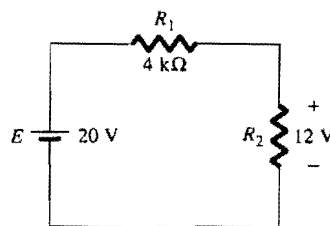


FIG. 2.61

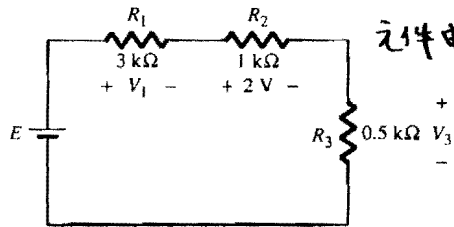


FIG. 2.62

元件电流相等

43. Determine the voltage levels  $V_1$  and  $V_3$  and  $E$  for the circuit in Fig. 2.62.

$$\frac{V_1}{R_1} = \frac{2V}{R_2} \rightarrow V_1 = 6V$$


$$\frac{V_3}{R_3} = \frac{2V}{R_2} \rightarrow V_3 = 1V$$

} 比例, 也代表电流相等。


$$E = V_1 + V_2 + V_3 = 9V$$

SECTION 2.10 Parallel Dc Networks

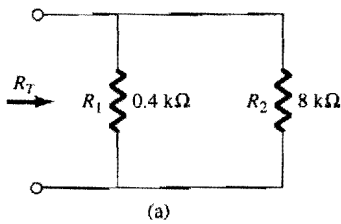44. Determine the total resistance of the networks in Fig. 2.63.



(a)

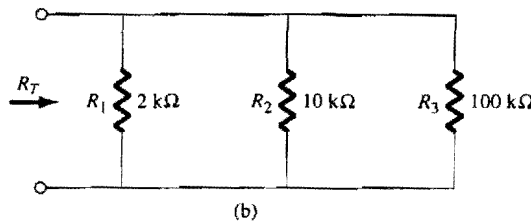

(b)


FIG. 2.63

$$R_T = R_1 \parallel R_2 \parallel R_3$$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = 610 \times 10^{-6} S$$


$$R_T = \frac{1}{610 \times 10^{-6} S} = 1.639 k\Omega$$

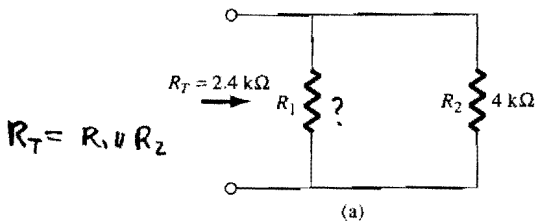45. Determine  $R_1$  for the networks in Fig. 2.64.



(a)

$$R_T = R_1 \parallel R_2$$

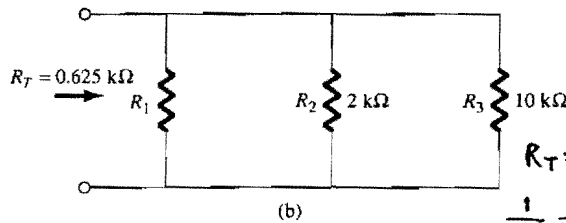

(b)

FIG. 2.64

$$R_T = R_1 \parallel R_2 \parallel R_3$$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$R_1 = 1 k\Omega$$

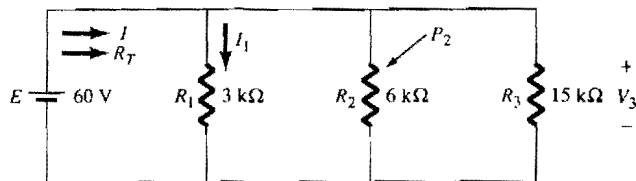


FIG. 2.65

46. For the network in Fig. 2.65 determine:


- $R_T = R_1 \parallel R_2 \parallel R_3$
- $I$
- $I_1$
- $V_3$
- $P_2$

- Total resistance  $R_T$   $\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$ ,  $R_T = 1.765 k\Omega$
- 由 E 出来的电流  $I = \frac{E}{R_T} = \frac{60V}{1.765 k\Omega} = 33.99 mA$
- 跨  $R_1, R_2, R_3$  的电流相等, 等于  $I$   
因此  $I_1 = \frac{V_{R1}}{R_1} = \frac{E}{R_1} = 20 mA$
- $V_3 = E = 60V$
- $P_2 = \frac{V_{R2}^2}{R_2} = \frac{(60V)^2}{6 k\Omega} = 0.6 W$

47. Determine the unknown quantities for the networks in Fig.

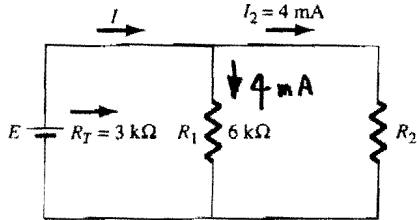2.66.


$$R_T = \frac{1}{\left(\frac{1}{R_1} + \frac{1}{R_2}\right)} = \frac{R_1 R_2}{R_1 + R_2} \quad 3 \text{ k}\Omega = \frac{(6 \text{ k}\Omega) R_2}{6 \text{ k}\Omega + R_2} \rightarrow R_2 = 6 \text{ k}\Omega$$



(a)

8.5 求  $R_2$  的  $V_2 = I_2 \times R_2 = 24 \text{ V}$   
 $E = V_2 = 24 \text{ V}$ ,  $I = \frac{E}{R_T} = 8 \text{ mA}$


FIG. 2.66

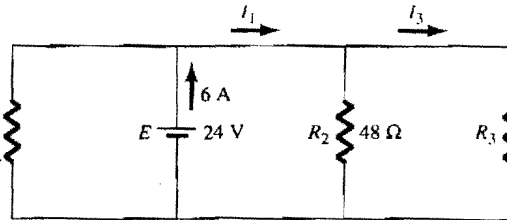


(b)

8.5  $R_1$  的  $V_1 = E = 24 \text{ V}$   
 $R_1$  的  $P_1 = \frac{V_1^2}{R_1}$   $64 \text{ W} = \frac{(24 \text{ V})^2}{R_1} \rightarrow R_1 = 9 \Omega$   
 由  $E$  流出的电流  $I = \frac{E}{R_T} \rightarrow R_T = 4 \Omega$   
 $\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \rightarrow R_3 = 8.471 \Omega$

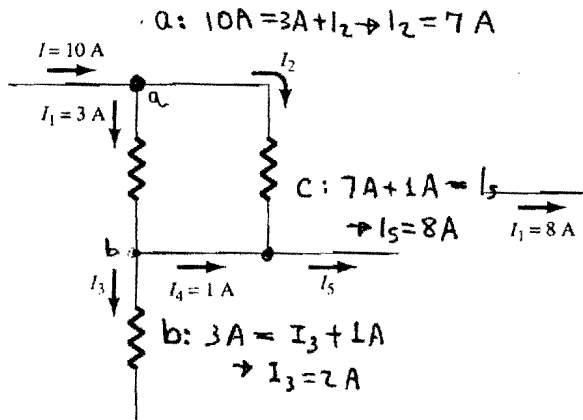48. Determine the unknown currents for the circuits in Fig. 2.67 using Kirchhoff's current law.



(a)

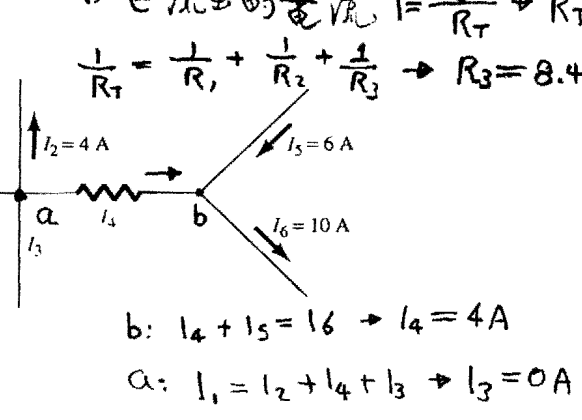

(b)

$a: 10 \text{ A} = 3 \text{ A} + I_2 \rightarrow I_2 = 7 \text{ A}$   
 $c: 7 \text{ A} + 1 \text{ A} = I_5 \rightarrow I_5 = 8 \text{ A}$   
 $b: 3 \text{ A} = I_3 + 1 \text{ A} \rightarrow I_3 = 2 \text{ A}$

$b: I_4 + I_5 = 16 \rightarrow I_4 = 4 \text{ A}$   
 $a: I_1 = I_2 + I_4 + I_3 \rightarrow I_1 = 0 \text{ A}$

FIG. 2.67

49. Determine the currents  $I_1$  and  $I_2$  in Fig. 2.68 using the current-divider rule. What is the ratio  $R_1/R_2$ ? How does it compare with the ratio  $I_1/I_2$ ?

$$I_1 = I \times \frac{R_2}{R_1 + R_2} = 10 \text{ mA} \times \frac{40 \text{ k}\Omega}{40 \text{ k}\Omega + 8 \text{ k}\Omega} = 8.333 \text{ mA}$$

$$I_2 = I - I_1 = 1.667 \text{ mA}$$

$$\frac{R_1}{R_2} = \frac{I_2}{I_1}$$

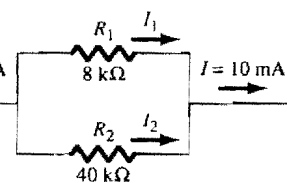


FIG. 2.68

50. Determine  $R_1$  for the network in Fig. 2.69 using the current-divider rule.

Current-divider rule  $I_{R_2} = I - I_1 = 12 \text{ A} - 4 \text{ A} = 8 \text{ A}$

$$I_1 = I \times \frac{R_2}{R_1 + R_2} \rightarrow R_1 = 16 \text{ k}\Omega$$

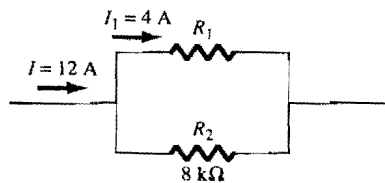


FIG. 2.69

51. Find  $I_1$ ,  $I_3$ , and  $I$  for the network in Fig. 2.70.

$$V_2 = I_2 \times R_2 = (2 \text{ mA})(4 \text{ k}\Omega) = 8 \text{ V}$$

$$V_1 = V_2, \quad V_3 = V_2$$

$$I_1 = \frac{V_1}{R_1} = \frac{8 \text{ V}}{1 \text{ k}\Omega} = 8 \text{ mA}$$

$$I_3 = \frac{V_3}{R_3} = \frac{8 \text{ V}}{0.1 \text{ k}\Omega} = 80 \text{ mA}$$

$$I = I_1 + I_2 + I_3 = 90 \text{ mA}$$

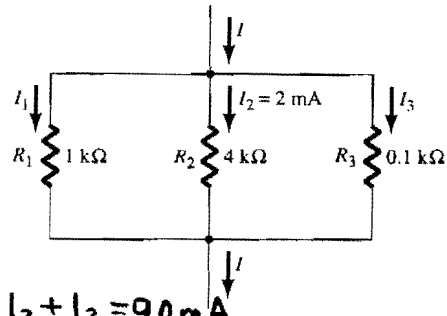


FIG. 2.70

**SECTION 2.12 Meter Considerations**

- Sketch the location and connections of ammeters and voltmeters used to measure the currents  $I_1$  and  $I_3$  and voltages  $V_1$  and  $V_3$  in Fig. 2.71.
- Using a voltmeter with an ohm-per-volt rating of 1000, determine the indication of the meter when it is placed across the 4-k $\Omega$  resistor if the 50-V scale is used.
- Repeat part (b) for a meter employing an ohm-per-volt rating of 20,000.
- Repeat part (b) for a DMM with an internal resistance of 11 M $\Omega$ .
- Show the connection for a wattmeter reading the power delivered to  $R_3$  and  $R_4$ .


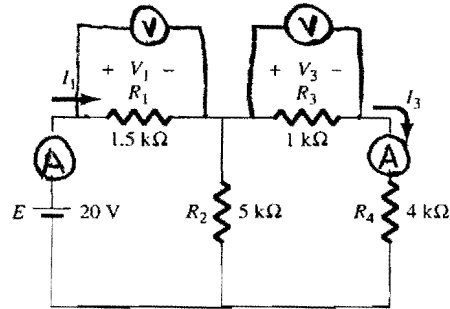


FIG. 2.71

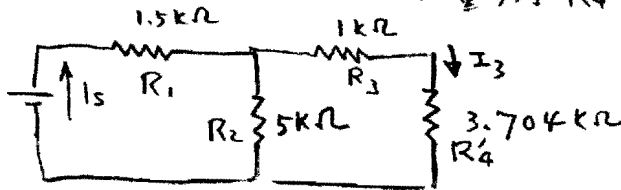b. Voltmeter 額定 (內部電阻) 1000  $\Omega/V$   
 若 Scale 定於 50V, 則內部電阻為 50 k $\Omega$   
 把 Voltmeter 電壓到  $R_4$  量測  $R_4$  的電壓降



$$R_4 \rightarrow R_4 \parallel R_v = 4 \text{ k}\Omega \parallel 50 \text{ k}\Omega = 3.704 \text{ k}\Omega = R_4'$$

$$R_T = \left[ \left( \underbrace{(R_4 \parallel R_v) + R_3}_{3.704} \right) \parallel R_2 \right] + R_1 = 3.924 \text{ k}\Omega$$

2.424 k $\Omega$

電壓源出來的電流  $I_s = \frac{E}{R_T} = \frac{20 \text{ V}}{3.924 \text{ k}\Omega} = 5.097 \text{ mA}$

$$I_3 = I_s \times \frac{R_2}{\underbrace{(R_4 \parallel R_v) + R_3 + R_2}_{4.704 \text{ k}\Omega}} = 2.626 \text{ mA}$$

$$V_{4 \text{ k}\Omega} = I_3 \times (R_4 \parallel R_v) = (2.626 \text{ mA})(3.704 \text{ k}\Omega) = 9.73 \text{ V}$$

(c) Voltmeter 額定為 20,000  $\Omega/V$   
 內部電阻  $R_v = 50 \text{ V} \times 20,000 \Omega/V = 1 \text{ M}\Omega$   
 重複前述程序  $\rightsquigarrow V_{4 \text{ k}\Omega} = 10 \text{ V}$