

電工作業第二章
2012版（雙號題）

謝志誠

Exercise 1

- If 24×10^{16} electrons pass through a conductor in $\frac{1}{2}$ min. determine: a. Charge in coulombs. b. Current.

$$\text{a. } 24 \times 10^{16} \text{ electrons} \times \frac{1.6 \times 10^{-19} \text{ coulombs}}{1 \text{ electron}} = 38.45 \times 10^{-3} \text{ coulombs}$$

$$\text{b. Current} = \frac{Q}{t} = \frac{38.45 \times 10^{-3} \text{ C}}{30 \text{ s}} = 1.282 \text{ mA}$$

Exercise 2

- How long will it take 1600 mC to pass through a copper conductor if the current is 0.5 A ?

$$I = \frac{Q}{t}$$

$$t = \frac{Q}{I} = \frac{1600\text{mC}}{0.5\text{A}} = 3.2\text{s}$$

Exercise 3

- How much charge has passed through a conductor if the current is $16 \mu\text{A}$ for 10 s ?

$$\text{Charge } Q = It = (16\mu\text{A})(10\text{s}) = 160\mu\text{C}$$

Exercise 4

- For a current of 1 mA, how many electrons will pass a particular point in the circuit in 1 s ? Write the number out of in full decimal form (all the zeros). Is it a significant number for such a small current level ?

$$\text{Charge } Q = It = (1\text{mA})(1\text{s}) = 1\text{mC} = 1 \times 10^{-3} \text{C}$$

每個電子帶 1.6×10^{-19} Coulombs ,
相對之下，每個 coulomb 含有 6.242×10^{18} 個電子。
所以，

$$1 \times 10^{-3} \text{C} \times \frac{6.242 \times 10^{18} \text{ electrons}}{1\text{C}} = 6.242 \times 10^{15} \text{ electrons}$$

Exercise 5

□ Write the following quantities in the most convenient form using the prefixes in Table 2.1.

- a. $0.05 \text{ A} = 50 \text{ mA}$
- b. $0.0004 \text{ V} = 0.4 \text{ mV}$
- c. $3 \times 10^4 \text{ V} = 10 \text{ kV}$
- d. $1200 \text{ V} = 1.2 \text{ kV}$
- e. $0.0000007 \text{ A} = 0.7 \mu\text{A}$
- f. $32,000,000 \text{ V} = 32 \text{ MV}$

| | |
|--|-----------------|
| $1,000,000,000,000 = 10^{12}$ | = terra = T |
| $1,000,000,000 = 10^9$ | = giga = G |
| $1,000,000 = 10^6$ | = mega = M |
| $1000 = 10^3$ | = kilo = k |
| $\frac{1}{1000} = 0.001 = 10^{-3}$ | = milli = m |
| $\frac{1}{1,000,000} = 0.000001 = 10^{-6}$ | = micro = μ |
| $0.000000001 = 10^{-9}$ | = nano = n |
| $0.000000000001 = 10^{-12}$ | = pico = p |

Exercise 6

□ What is the resistance of 1000 ft of No. 12 house wire?

No.12者，每1,000 ft電阻1.588 Ω。因此，1000 ft的電線的電阻為 1.588 Ω。

$$R = 1,000\text{ft} \times \frac{1.588\Omega}{1000\text{ft}} = 1.588\Omega$$

Exercise 7

□ What is the area in circular mils of wires having the following diameters?

a. 1/32 in

$$a. \quad d = \frac{1}{32} \text{ in} = 0.03125 \text{ in} \quad d_{\text{mils}} = 31.25 \text{ mils}$$

b. 0.01 ft

c. 0.1 cm

$$A_{\text{CM}} = (d_{\text{mils}})^2 = 976.56 \text{ CM}$$

$$b. \quad d = 0.01 \text{ ft} = 0.12 \text{ in} \quad d_{\text{mils}} = 120 \text{ mils}$$

$$A_{\text{CM}} = (d_{\text{mils}})^2 = 14,400 \text{ CM}$$

$$c. \quad d = 0.1 \text{ cm} = 0.03937 \text{ in} \quad d_{\text{mils}} = 39.37 \text{ mils}$$

$$A_{\text{CM}} = (d_{\text{mils}})^2 = 1,550 \text{ CM}$$

Exercise 8

□ What is the diameter in inches of wires having the following areas in circular mils?

a. 10,000 CM

b. 625 CM

c. 50,000 CM

a. $d_{\text{mils}} = \sqrt{10,000\text{CM}} = 100\text{mils}$ $d = 0.1\text{in}$

b. $d_{\text{mils}} = \sqrt{625\text{CM}} = 25\text{mils}$ $d = 0.025\text{in}$

c. $d_{\text{mils}} = \sqrt{50,000\text{CM}} = 223.61\text{mils}$ $d = 0.2236\text{in}$

Exercise 9

- Determine the energy expended (in joules) to bring a charge of 40 mC through a potential difference of 120 V.

推動40 mC的電荷跨越120 V的電位差，能量要用多少？

$$W = VQ = (120\text{V})(40\text{mC}) = 4.8\text{Joules}$$

Exercise 10

- What is the potential difference between two points in an electric circuit if 200 mJ of energy is required to bring a charge of 40 μC from one point to the other?

在多大的電位差下，推動40 μC 的電荷
需要使用200 mJ的能量？

$$W = VQ$$

$$V = \frac{W}{Q} = \frac{200\text{mJ}}{40\mu\text{C}} = 5\text{kV}$$

Exercise 11

- How much energy is required to move 18×10^{18} electrons through a potential difference of 12 V?

推動 18×10^{18} 個電子跨越 12V 的電位差，能量要用多少？
先算出 18×10^{18} 個電子帶有多少電荷，

$$Q = 18 \times 10^{18} \text{ electrons} \times \frac{1.6 \times 10^{-19} \text{ C}}{\text{electron}} = 2.88 \text{ C}$$

$$W = VQ = (12 \text{ V})(2.88 \text{ C}) = 34.6 \text{ Joules}$$

Exercise 12

- How much energy is expended to maintain a current of 10 mA between two points in an electric circuit for 5 s if the potential difference between two points is 20 mV?

電位差20 mV下，推動10 mA的電流達5 seconds，
需要多少的能量？

先求出推動的電荷量.....

Q?

$$Q = It = (10\text{mA})(5\text{s}) = 50\text{mC}$$

$$W = VQ = (20\text{mV})(50\text{mC}) = 1\text{mJ}$$

Exercise 13

- Determine the internal resistance of a battery-operated clock if a current of 1.8 mA results from an applied voltage of 1.5 V.

利用歐姆定律 Ohm's law

$$R = \frac{E}{I} = \frac{1.5V}{1.8mA} = 833.33\Omega$$

電源電壓，使用符號E，非V

Exercise 14

- Determine the current through a soldering iron if 120 V is applied. The iron has a resistance of 18Ω .

利用歐姆定律 Ohm's law

$$I = \frac{E}{R} = \frac{120V}{18\Omega} = 6.67A$$

Exercise 15

- Determine the voltage drop across a $2.2 \text{ M}\Omega$ resistor with a current of $30 \text{ }\mu\text{A}$ pass through it. What resistance would be required to limit the current to 1.5 A if the applied voltage is 64 V ?

跨越 $2.2 \text{ M}\Omega$ 電阻的電壓降 V

$$V = RI = (2.2\text{M}\Omega)(30\mu\text{A}) = 66\text{V}$$

若施予的電壓為 64 V ，電流限於 1.5 A ，
則使用的電阻的電阻值

$$R = \frac{V}{I} = \frac{64\text{V}}{1.5\text{A}} = 42.67\Omega$$

Exercise 16

□ Determine the resistance of 50 ft of 1/16-in. diameter copper wire.

先求1/16in為多少 A_{CM} ?

$$d_{\text{mils}} = 62.5 \text{mils}$$

$$A_{CM} = (d_{\text{mils}})^2 = 3,906.25 \text{CM}$$

$$R = \rho \frac{\ell}{A} = (10.37 \text{CM} - \Omega / \text{ft}) \frac{(50 \text{ft})}{3,906.25 \text{CM}} = 132.74 \text{m}\Omega$$

↑ ρ 的單位

Exercise 17

□ Calculate the resistance of 600 ft of No 14 wire using Table 2.2.

No.14者，每1,000 ft電阻 2.525 Ω。因此，600 ft的電線的電阻為

$$R = 600\text{ft} \times \frac{2.525\Omega}{1000\text{ft}} = 1.515\Omega$$

| AWG No. | Area (CM) | Ω/1000 ft at 20°C | Maximum Allowable Current for RHW Insulation (A) [†] | AWG No. | Area (CM) | Ω/1000 ft at 20°C |
|---------|-----------|-------------------|---|---------|-----------|-------------------|
| 0000 | 211,600 | 0.0490 | 360 | 19 | 1288.1 | 8.051 |
| 000 | 167,810 | 0.0618 | 310 | 20 | 1021.5 | 10.15 |
| 00 | 133,080 | 0.0780 | 265 | 21 | 810.10 | 12.80 |
| 0 | 105,530 | 0.0983 | 230 | 22 | 642.40 | 16.14 |
| 1 | 83,694 | 0.1240 | 195 | 23 | 509.45 | 20.36 |
| 2 | 66,373 | 0.1563 | 170 | 24 | 404.01 | 25.67 |
| 3 | 52,634 | 0.1970 | 145 | 25 | 320.40 | 32.37 |
| 4 | 41,742 | 0.2485 | 125 | 26 | 254.10 | 40.81 |
| 5 | 33,102 | 0.3133 | — | 27 | 201.50 | 51.47 |
| 6 | 26,250 | 0.3951 | 95 | 28 | 159.79 | 64.90 |
| 7 | 20,816 | 0.4982 | — | 29 | 126.72 | 81.83 |
| 8 | 16,509 | 0.6282 | 65 | 30 | 100.50 | 103.2 |
| 9 | 13,094 | 0.7921 | — | 31 | 79.70 | 130.1 |
| 10 | 10,381 | 0.9989 | 40 | 32 | 63.21 | 164.1 |
| 11 | 8,234.0 | 1.260 | — | 33 | 50.13 | 206.9 |
| 12 | 6,529.9 | 1.588 | 25 | 34 | 39.75 | 260.9 |
| 13 | 5,178.4 | 2.003 | — | 35 | 31.52 | 329.0 |
| 14 | 4,106.8 | 2.525 | 20 | 36 | 25.00 | 414.8 |
| 15 | 3,256.7 | 3.184 | — | 37 | 19.83 | 523.1 |
| 16 | 2,582.9 | 4.016 | — | 38 | 15.72 | 659.6 |
| 17 | 2,048.2 | 5.064 | — | 39 | 12.47 | 831.8 |
| 18 | 1,624.3 | 6.385 | — | 40 | 9.89 | 1049.0 |

From the 1965 National Electrical Code, © published by the National Fire Protection Association.

Exercise 18

- Determine the diameter (in inches) of a copper inductor having a length of 200 ft and a resistance of 0.2Ω .

$$R = \rho \frac{\ell}{A} \rightarrow$$

$$A_{\text{CM}} = \rho \frac{\ell}{R} = (10.37\text{CM} - \Omega/\text{ft}) \frac{(200\text{ft})}{0.2\Omega} = 10,370\text{CM}$$

$$d_{\text{mils}} = \sqrt{10,370\text{CM}} = 101.83\text{mils}$$

$$d = 0.102\text{in}$$

Exercise 19

□ What is the resistance of 1 mi of No.12 house wire? How does it compare with the resistance of 1 kΩ connected to the end the conductor?

| AWG No. | Area (CM) | Ω/1000 ft at 20°C | Maximum Allowable Current for RHW Insulation (A) [†] | AWG No. | Area (CM) | Ω/1000 ft at 20°C |
|---------|-----------|-------------------|---|---------|-----------|-------------------|
| 0000 | 211,600 | 0.0490 | 360 | 19 | 1288.1 | 8.051 |
| 000 | 167,810 | 0.0618 | 310 | 20 | 1021.5 | 10.15 |
| 00 | 133,080 | 0.0780 | 265 | 21 | 810.10 | 12.80 |
| 0 | 105,530 | 0.0983 | 230 | 22 | 642.40 | 16.14 |
| 1 | 83,694 | 0.1240 | 195 | 23 | 509.45 | 20.36 |
| 2 | 66,373 | 0.1563 | 170 | 24 | 404.01 | 25.67 |
| 3 | 52,634 | 0.1970 | 145 | 25 | 320.40 | 32.37 |
| 4 | 41,742 | 0.2485 | 125 | 26 | 254.10 | 40.81 |
| 5 | 33,102 | 0.3133 | — | 27 | 201.50 | 51.47 |
| 6 | 26,250 | 0.3951 | 95 | 28 | 159.79 | 64.90 |
| 7 | 20,816 | 0.4982 | — | 29 | 126.72 | 81.83 |
| 8 | 16,509 | 0.6282 | 65 | 30 | 100.50 | 103.2 |
| 9 | 13,094 | 0.7921 | — | 31 | 79.70 | 130.1 |
| 10 | 10,381 | 0.9989 | 40 | 32 | 63.21 | 164.1 |
| 11 | 8,234.0 | 1.260 | — | 33 | 50.13 | 206.9 |
| 12 | 6,529.9 | 1.588 | 25 | 34 | 39.75 | 260.9 |
| 13 | 5,178.4 | 2.003 | — | 35 | 31.52 | 329.0 |
| 14 | 4,106.8 | 2.525 | 20 | 36 | 25.00 | 414.8 |
| 15 | 3,256.7 | 3.184 | — | 37 | 19.83 | 523.1 |
| 16 | 2,582.9 | 4.016 | — | 38 | 15.72 | 659.6 |
| 17 | 2,048.2 | 5.064 | — | 39 | 12.47 | 831.8 |
| 18 | 1,624.3 | 6.385 | — | 40 | 9.89 | 1049.0 |

From the 1965 National Electrical Code. © published by the National Fire Protection Association.

No.12者，每1,000 ft 電阻1.588 Ω。因此，1 mi的電線的電阻為（1 mi = 5,280 ft）

$$R = 5,280\text{ft} \times \frac{1.588\Omega}{1000\text{ft}} = 8.38\Omega \ll 1\text{k}\Omega$$

Exercise 20

- If the resistance of a copper conductor is $2\ \Omega$ at room temperature ($T = 20^\circ\text{C}$), what is its resistance at 100°C (the boiling point of water)?

$$\frac{T + t_1}{R_1} = \frac{T + t_2}{R_2}$$
$$\frac{234.5 + 20}{2\ \Omega} = \frac{234.5 + 100}{R_2}$$
$$R_2 = \frac{334.5(20)}{254.5} = 2.63\ \Omega$$

Exercise 21

- At what temperature will the resistance of a No. 8 copper wire double if its resistance at $T = 20^\circ\text{C}$ is $1\ \Omega$?

$$\frac{T + t_1}{R_1} = \frac{T + t_2}{R_2}$$

$$\frac{234.5 + 20}{1\Omega} = \frac{234.5 + t_2}{2\Omega}$$

$$t_2 = 234.5^\circ\text{C}$$

Exercise 22

- If the resistance of a copper conductor 400 ft long is 10Ω at room temperature ($T = 20^\circ\text{C}$), what is its resistance at -20°C ?

$$\frac{T + t_1}{R_1} = \frac{T + t_2}{R_2}$$

$$\frac{234.5 + 20}{10\Omega} = \frac{234.5 - 20}{R_2}$$

$$R_2 = \frac{214.5(10)}{254.5} = 8.43\Omega$$

Exercise 23

- a. Determine the resistance of a modeled composition resistor with the following color bands: red, red, brown, gold.
- b. Indicate its expected range of values.

a. Resistance is $220\ \Omega \pm 5\%$

b. Expected range of values: $209\ \Omega \sim 231\ \Omega$

Exercise 24

- Determine the color bands of a $100 \text{ k}\Omega$ resistor with a tolerance of 5%.

$$100 \text{ k}\Omega = 10 \times 10^4$$

brown/black/yellow/Gold

Exercise 25

- Determine the color bands of a 3,952 Ω resistor with a tolerance of 10%.

orange/white/gold/silver

橙、白、金、銀

Exercise 26

- Determine the power delivered by a 12 V battery at a current drain of 240 mA.

$$P = EI = (12\text{V})(240\text{mA}) = 2.88\text{W}$$

Exercise 28

- A 280 W television set is connected to a 120 V outlet.
Determine the current drawn by the set.

$$P = EI$$

$$I = \frac{P}{E} = \frac{280\text{W}}{120\text{V}} = 2.33\text{A}$$

Exercise 30


□ Calculate the cost of using the following appliances for the indicated time period if the unit cost is 9 cents/kWh.

a. Six 60 -W bulbs for 6 h.

b. 8-W clock for 30 days (1 month).

c. 160-W television set for 4 h 30 min.

d. 5000-W clothes dryer for 45 min.


$$\text{kWh} = \sum = \frac{(6)(60\text{W})(6\text{h}) + (8\text{W})(30\text{days})(24\text{h} / \text{day})}{1000} +$$

$$\frac{(160\text{W})(4.5\text{h}) + (5000\text{W})(3/4\text{h})}{1000} = 12.39\text{kWh}$$

$$\text{Cost} = (12.39\text{kWh})(9\text{cents} / \text{kWh}) = 111.51\text{cents}$$

Exercise 32

- How long can we use a welding unit for \$1.00 if the unit draws 14 A at 220 V and the cost is 9 cents/kWh?

\$1.00使用多少kWh？

$$\frac{\$1.00}{9\text{cents/kWh}} = \frac{100\text{cents}}{9\text{cents/kWh}} = 11.11\text{kWh}$$

$$\text{kWh} = \frac{Pt}{1000} \rightarrow 11.11\text{kWh} = \frac{(220\text{V})(14\text{A})t}{1000}$$

$$\Rightarrow t = 3.61\text{h}$$

Exercise 34

- a. A 2.2-hp motor has an input power demand of 2,400 W. Determine its efficiency.
- b. If the applied voltage is 120 V, find the input current.
- c. What is the power lost in the energy transfer (in watts)?



$$\text{a. } \eta = \frac{P_o}{P_i} = \frac{(2.2\text{hp})(746\text{W / hp})}{2,400\text{W}} \times 100\% = 68.4\%$$

$$\text{b. } P_i = EI \quad I = \frac{P_i}{E} = \frac{2,400\text{W}}{120\text{V}} = 20\text{A}$$

$$\text{c. Power lost} = P_i - P_o = 2400\text{W} - 1641\text{W} = 759\text{W}$$

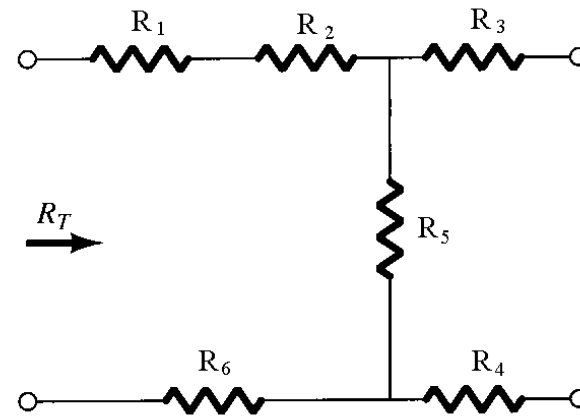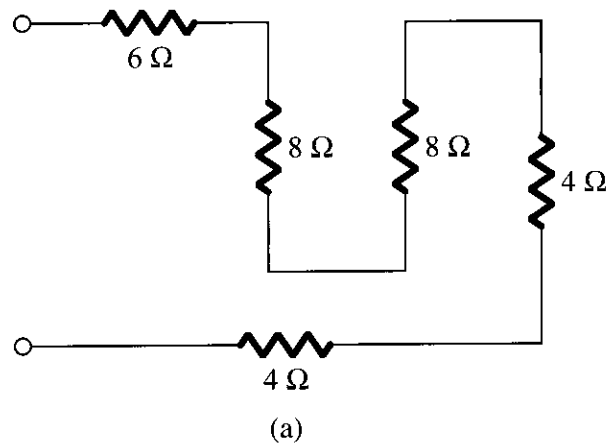Exercise 36

□ Find the total resistance of the networks in Fig. 2.55.



a. $R_T = 6\ \Omega + 8\ \Omega + 8\ \Omega + 4\ \Omega + 4\ \Omega = 30\ \Omega$

b. $R_T = R_1 + R_2 + R_5 + R_6$

Exercise 38

□ For the circuit in Fig. 2.57, determine:

- a. R_T .
- b. I .
- c. V_3 .
- d. P_2 .

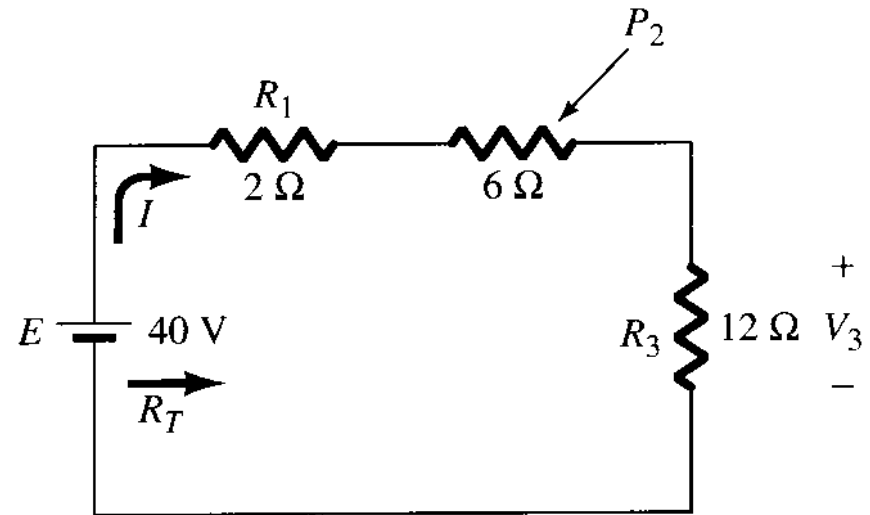


FIG. 2.57

a. $R_T = 2\Omega + 6\Omega + 12\Omega = 20\Omega$

b. $I = \frac{E}{R_T} = \frac{40V}{20\Omega} = 2A$

c. $V_3 = IR_3 = (2A)(12\Omega) = 24V$

d. $P_2 = I^2R_2 = (2A)^2(6\Omega) = 24W$

Exercise 39-a


- Determine the unknown quantities for the networks in Fig. 2.58a.

$$P = I^2 R_3 = 16\text{W} \rightarrow I = 2\text{A}$$

$$R_1 = \frac{8\text{V}}{2\text{A}} = 4\Omega$$

$$R_T = R_1 + R_2 + R_3 = 11\Omega$$

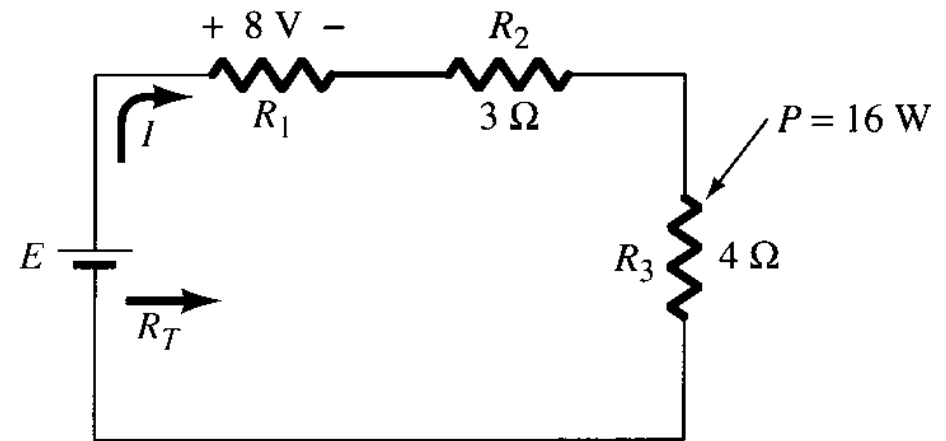
$$E = I \times R_T = (2\text{A})(11\Omega) = 22\text{V}$$



(a)

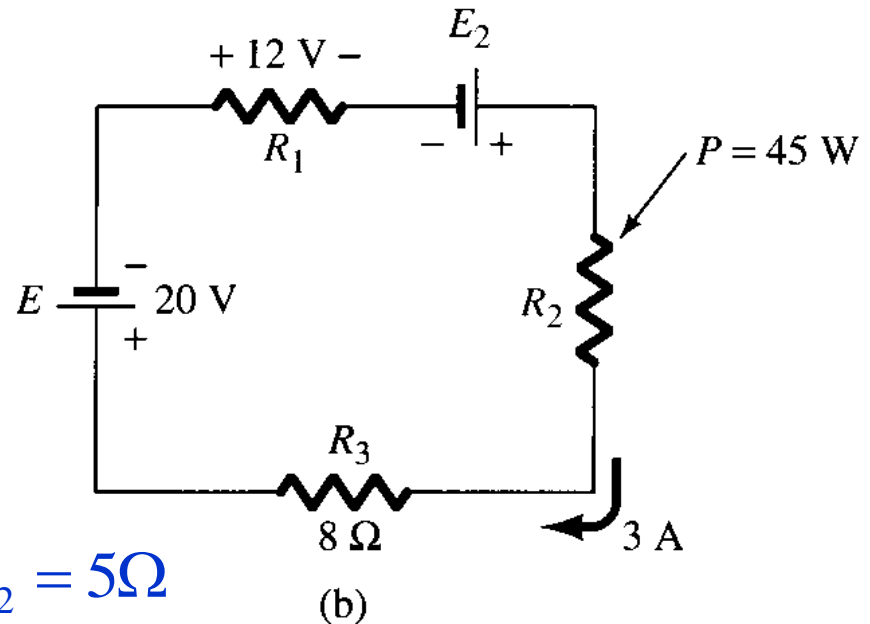Exercise 39-b

- Determine the unknown quantities for the networks in Fig. 2.58b.



$$P = I^2 R_2 = 9 \times R_2 = 45\text{W} \rightarrow R_2 = 5\Omega$$

$$R_1 = \frac{12\text{V}}{3\text{A}} = 4\Omega$$

$$R_T = R_1 + R_2 + R_3 = 17\Omega$$

$$E_2 - 20\text{V} = I \times R_T = (3\text{A})(17\Omega) = 51\text{V}$$

$$E_2 = 71\text{V}$$

Exercise 40-a


- Determine the unknown voltage for the circuit in Fig. 2.59 using Kirchhoff's voltage law.

$$16V - 5V + 12V - V_3 = 0$$

$$V_3 = 23V$$

$$V_4 = 16V - 5V = 11V$$

$$V_5 = V_3 = 23V$$

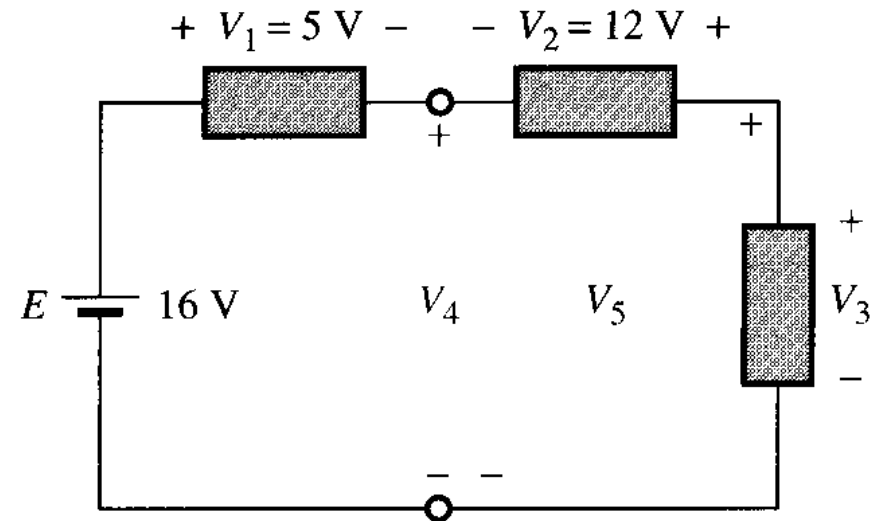

(a)


Exercise 40-6

- Determine the unknown voltage for the circuit in Fig. 2.59 using Kirchhoff's voltage law.

$$V_3 = E = 40\text{V}$$

$$40\text{V} - 16\text{V} - V_2 + 4\text{V} = 0$$
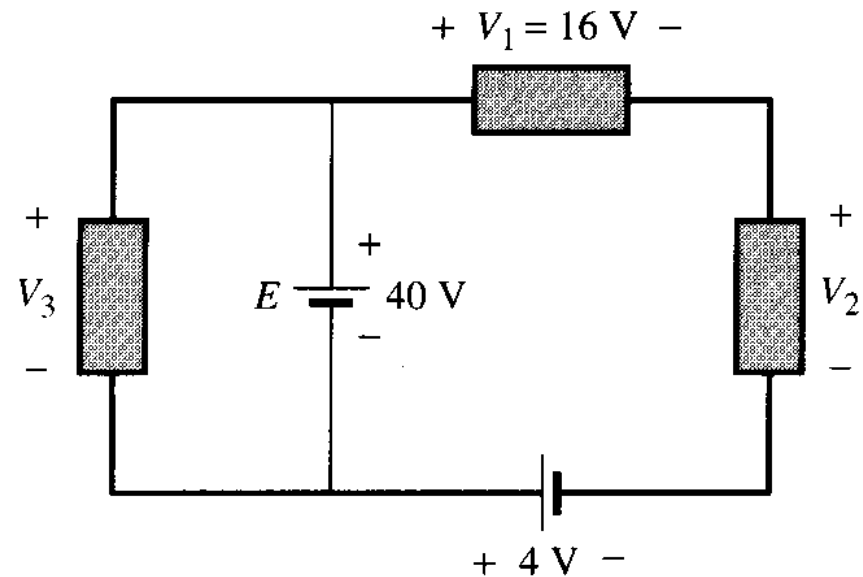
$$V_2 = 44\text{V} - 16\text{V} = 28\text{V}$$



(b)

Exercise 41

- Determine the voltage V_3 and V_4 using the voltage-divider rule for the network in Fig. 2.60.

$$V_3 = \frac{R_3}{R_1 + R_2 + R_3} \times E = 3.6V$$

$$V_4 = \frac{R_2 + R_3}{R_1 + R_2 + R_3} \times E = 9.6V$$

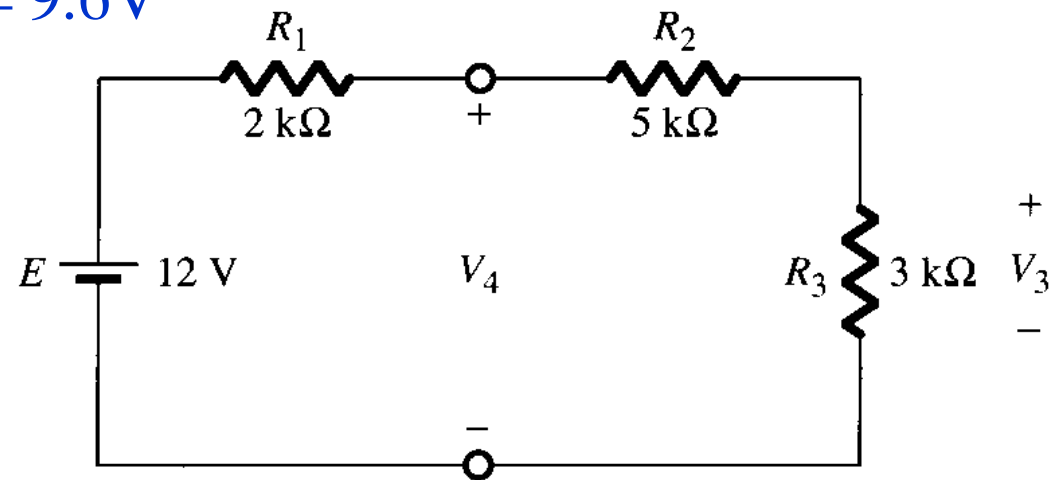


FIG. 2.60

Exercise 42

- Determine R_2 for the given voltage level for the network in Fig. 2.61 using the voltage-divider rule.

$$V_2 = \frac{R_2}{R_1 + R_2} \times E = 12\text{V}$$

$$R_2 = 6\text{k}\Omega$$

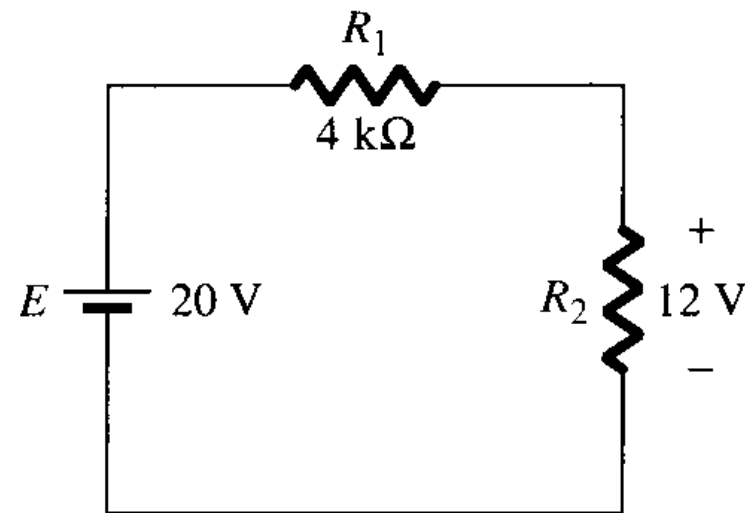


FIG. 2.61

Exercise 43

- Determine the voltage levels V_1 and V_3 and E for the circuit in Fig. 2.62.

$$\frac{V_1}{R_1} = \frac{2V}{R_2} \rightarrow V_1 = 6V$$

$$\frac{V_3}{R_3} = \frac{2V}{R_2} \rightarrow V_3 = 1V$$

$$E = V_1 + V_2 + V_3 = 9V$$


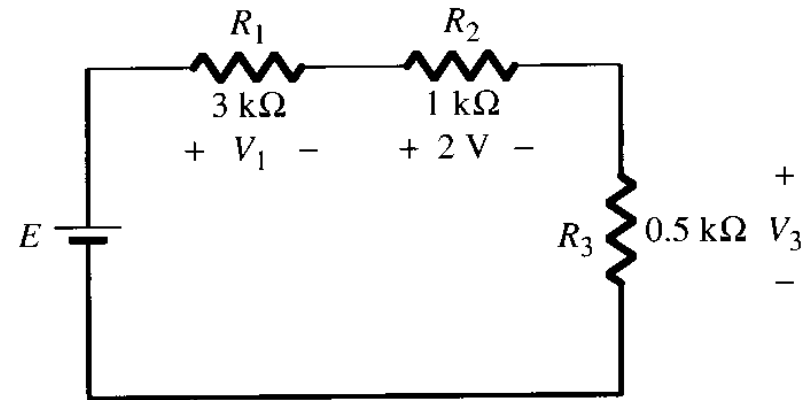



FIG. 2.62

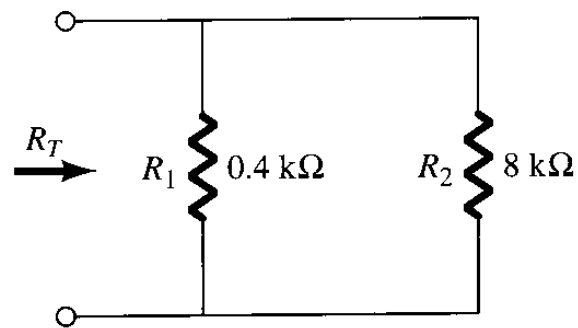Exercise 44

□ Determine the total resistance of the networks in Fig. 2.63.



(a)

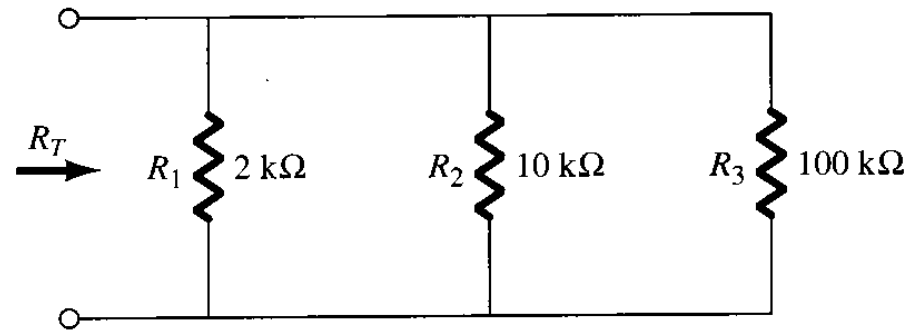

(b)


$$\text{a. } R_T = R_1 // R_2 = 0.4 \text{ k}\Omega // 8 \text{ k}\Omega = 380.95 \Omega \quad \frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\text{b. } R_T = R_1 // R_2 // R_3 = 2 \text{ k}\Omega // 10 \text{ k}\Omega // 100 \text{ k}\Omega = 1.639 \text{ k}\Omega$$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

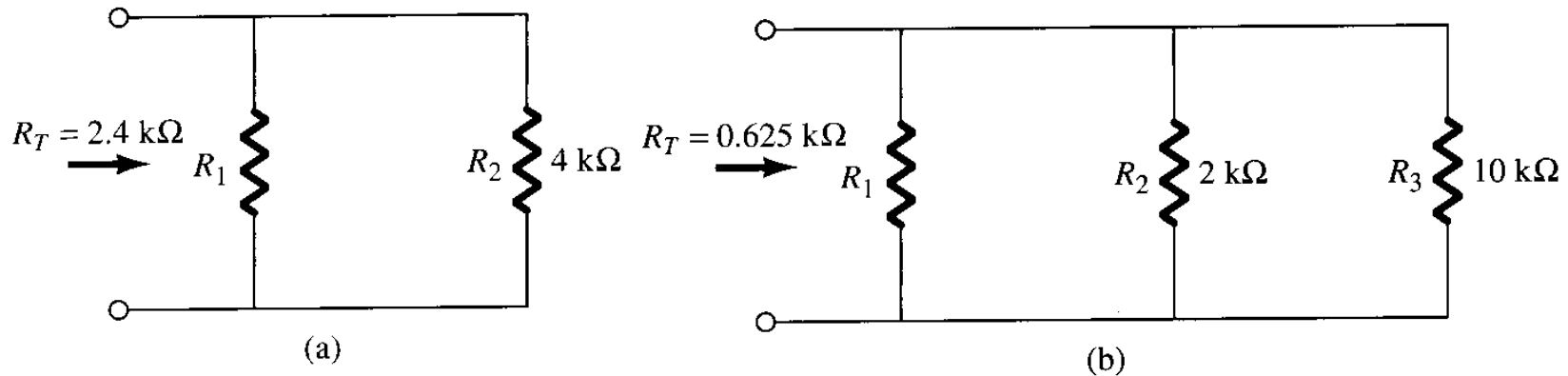Exercise 45

□ Determine R_1 for the networks in Fig. 2.64.



a. $R_T = R_1 // R_2 = R_1 // 4\text{k}\Omega = 2.4\text{k}\Omega$

$\rightarrow R_1 = 6\text{k}\Omega$

b. $R_T = R_1 // R_2 // R_3 = R_1 // 2\text{k}\Omega // 10\text{k}\Omega = 0.625\text{k}\Omega$

$\rightarrow R_1 = 1\text{k}\Omega$

Exercise 46-1

□ For the network in Fig. 2.65 determine:

- a. R_T . b. I . c. V_1 . d. V_3 . e. P_2 .

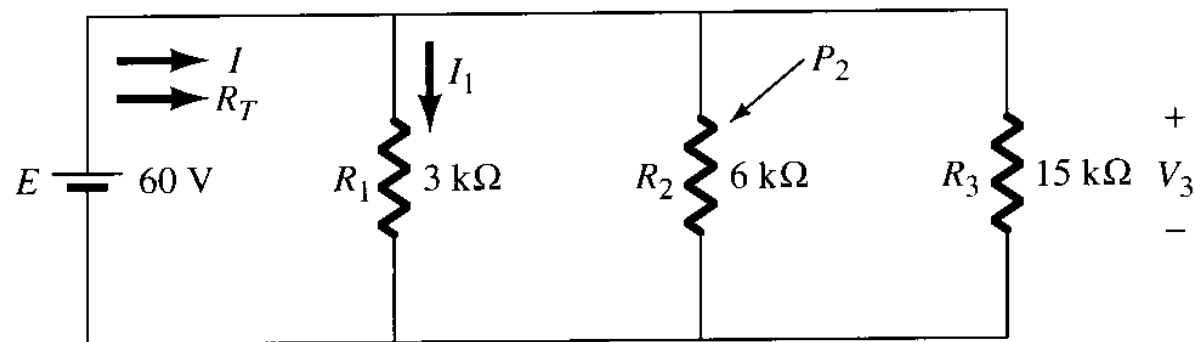


FIG. 2.65

a. $R_T = R_1 // R_2 // R_3 = 3\text{ k}\Omega // 6\text{ k}\Omega // 15\text{ k}\Omega = 1.765\text{ k}\Omega$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Exercise 46⁻²

□ For the network in Fig. 2.65 determine:

- a. R_T . b. I . c. V_1 . d. V_3 . e. P_2 .

$$\text{b. } I = \frac{E}{R_T} = \frac{60\text{V}}{1.765\text{k}\Omega} = 33.99\text{mA} \quad \text{c. } I_1 = \frac{V_{R_1}}{R_1} = \frac{E}{R_1} = 20\text{mA}$$

$$\text{c. } I_1 = \frac{V_{R_1}}{R_1} = \frac{E}{R_1} = 20\text{mA} \quad \text{d. } V_3 = E = 60\text{V}$$

$$\text{e. } P_2 = \frac{V_{R_2}^2}{R_2} = \frac{E^2}{R_2} = \frac{(60\text{V})^2}{6\text{k}\Omega} = 0.6\text{W}$$


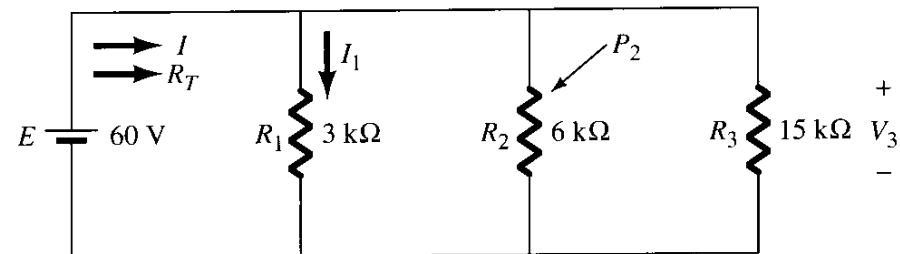


FIG. 2.65

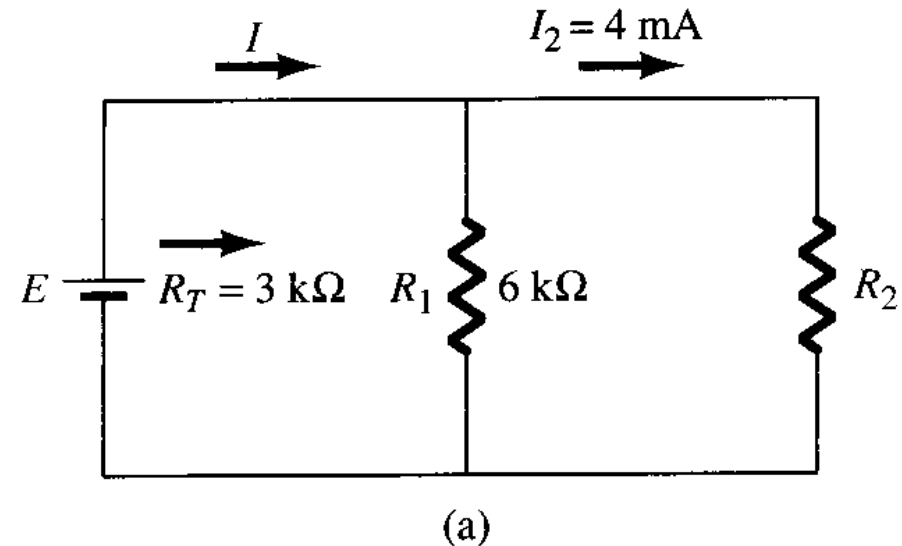Exercise 47-a

- Determine the unknown quantities for the networks in Fig. 2.66a.



$$R_T = R_1 // R_2 = 6 \text{ k}\Omega // R_1 = 3 \text{ k}\Omega \quad \rightarrow R_2 = 6 \text{ k}\Omega$$

$$V_2 = I_2 \times R_2 = (4 \text{ mA})(6 \text{ k}\Omega) = 24 \text{ V}$$

$$E = V_2 = 24 \text{ V} \quad I = \frac{E}{R_T} = 8 \text{ mA}$$

Exercise 47-b

□ Determine the unknown quantities for the networks in Fig. 2.66b.

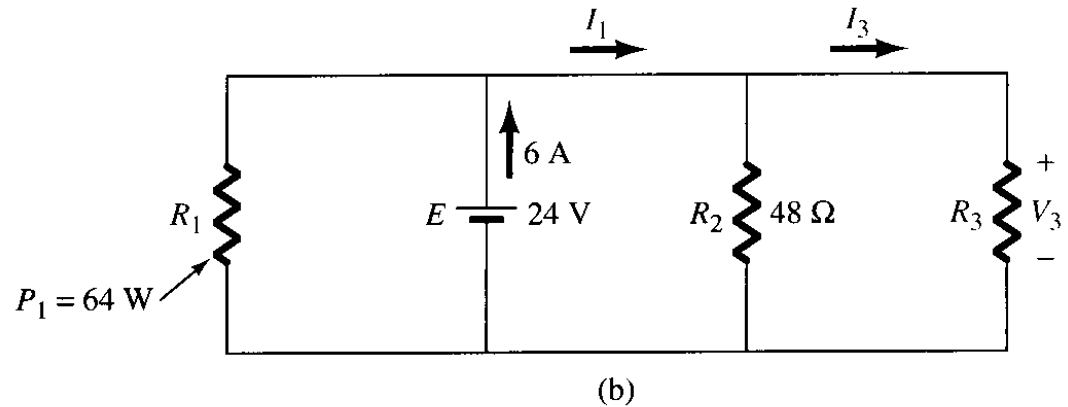


FIG. 2.66

$$V_1 = V_2 = V_3 = E = 24V \quad I_2 = \frac{V_2}{R_2} = \frac{24V}{48\Omega} = 0.5A$$

$$P_1 = \frac{V_1^2}{R_1} = 64W \rightarrow R_1 = 9\Omega \quad I = \frac{E}{R_T} = \frac{24V}{R_T} = 6A \rightarrow R_T = 4\Omega$$

$$R_T = R_1 // R_2 // R_3 = 4\Omega \rightarrow R_1 = 8.471\Omega$$

$$I_3 = \frac{V_3}{R_3} = \frac{24V}{8.471\Omega} = 2.833A \quad I_1 = I_2 + I_3 = 3.333A$$

Exercise 48

□ Determine the unknown currents for the circuits in Fig. 2.67 using Kirchhoff's current law.


a. $10\text{A} = 3\text{A} + I_2$

$$I_2 = 7\text{A} \quad I_2 + 1\text{A} = I_5 \quad I_5 = 8\text{A}$$


$$3\text{A} = I_3 + 1\text{A} \quad I_3 = 2\text{A}$$

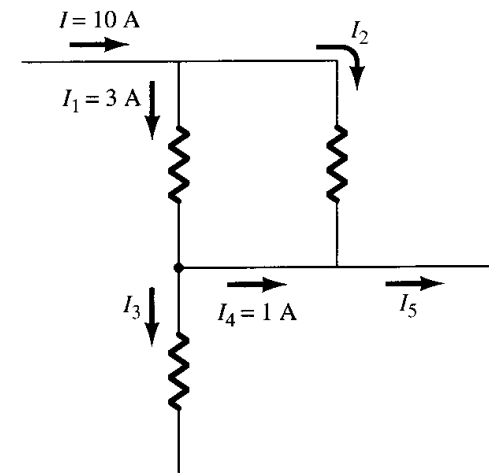b. $I_4 + I_5 = I_6 \quad I_4 + 6\text{A} = 10\text{A} \quad I_4 = 4\text{A}$

$$8\text{A} - 4\text{A} - 4\text{A} + I_3 = 0 \quad I_3 = 0\text{A}$$



(a)

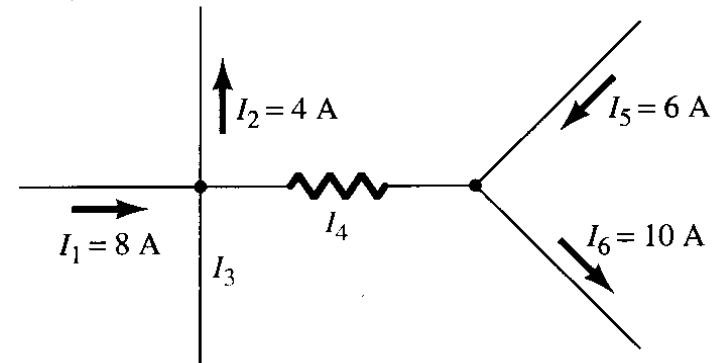

Exercise 49

- Determine the currents I_1 and I_2 in Fig. 2.68 using the current divider rule. What is the ratio R_1/R_2 ? How does it compare with the ratio I_1/I_2 ?

$$I_1 = I \times \frac{R_2}{R_1 + R_2} = 10\text{mA} \times \frac{40\text{k}\Omega}{8\text{k}\Omega + 40\text{k}\Omega} = 8.333\text{mA}$$

$$I_2 = I - I_1 = 1.667\text{mA}$$

$$\frac{R_1}{R_2} = \frac{I_2}{I_1}$$

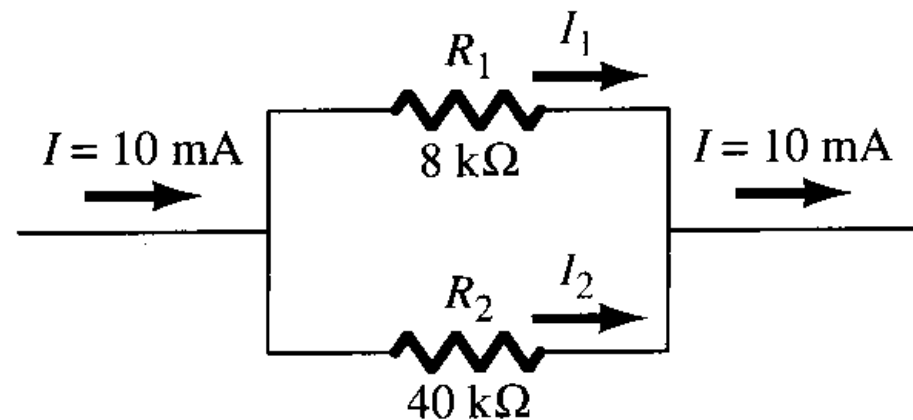


FIG. 2.68

Exercise 50

- Determine R_1 for the network in Fig. 2.69 using current-divider rule.

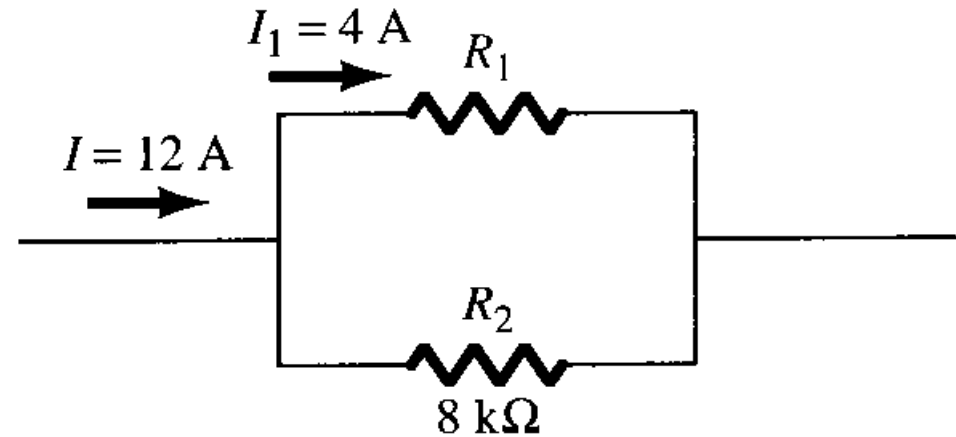


FIG. 2.69

$$I_{R_2} = I - I_1 = 12\text{ A} - 4\text{ A} = 8\text{ A}$$

$$V_{R_2} = I_{R_2} \times R_2 = (8\text{ A})(8\text{ k}\Omega) = 64\text{ kV}$$

$$R_1 = \frac{V_{R_1}}{I_1} = 16\text{ k}\Omega$$

Exercise 51

□ Find I_1 , I_3 , and I for the network in Fig. 2.70.

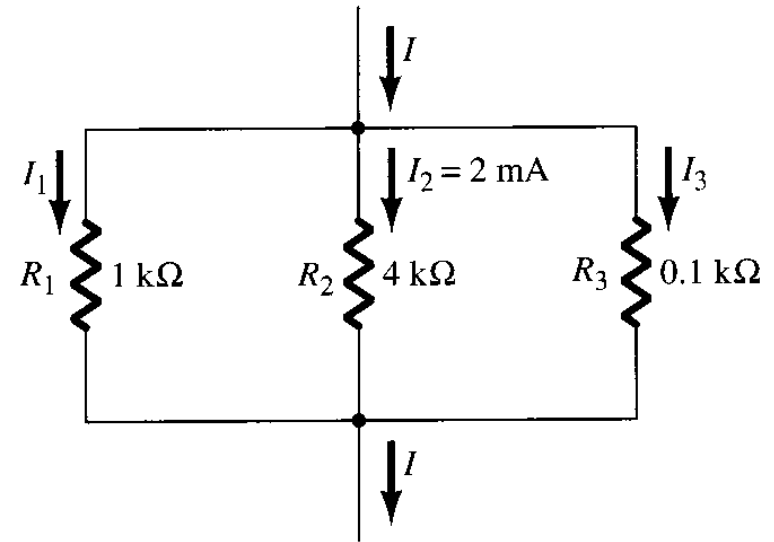


FIG. 2.70

$$V_2 = I_2 \times R_2 = (2\text{mA})(4\text{k}\Omega) = 8\text{V}$$

$$V_1 = V_2 \quad V_2 = V_3$$

$$I_1 = \frac{V_1}{R_1} = \frac{8\text{V}}{1\text{k}\Omega} = 8\text{mA}$$

$$I_3 = \frac{V_3}{R_3} = \frac{8\text{V}}{0.1\text{k}\Omega} = 80\text{mA}$$

$$I = I_1 + I_2 + I_3 = 90\text{mA}$$

Exercise 52

- a. Sketch the location and connecting of ammeters and voltmeters used to measure the currents I_1 and I_3 and voltages V_1 and V_3 in Fig. 2.71.
- b. Using a voltmeter with an ohm-per-volt rating of 1000, determine the indication of meter when it is placed across the $4\text{-k}\Omega$ resistor if the 50-V scale is used.
- c. Repeat part (b) for a meter employing an ohm-per-volt rating of 20,000.
- d. Repeat part (b) for a DMM with an internal resistance of $11\text{ M}\Omega$.
- e. Show the connection for a wattmeter reading the power delivered to R_3 and R_4 .

Exercise 52

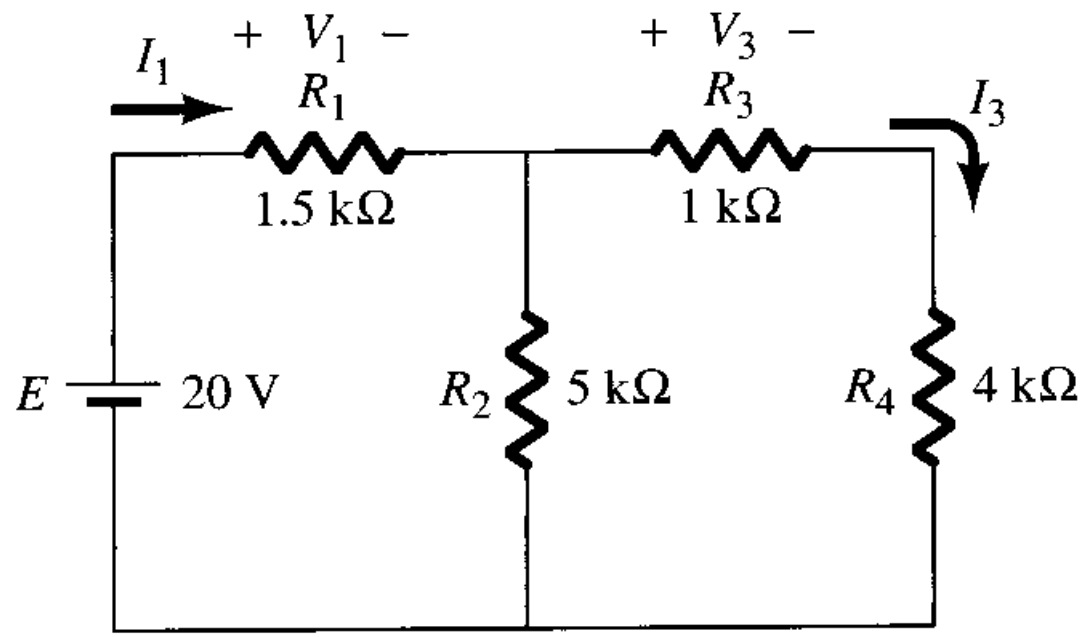


FIG. 2.71